

VLSI LAB MANUAL**Semester: VII****Subject code: 15ECL77****LIST OF EXPERIMENTS**

Sl. no	Name of the experiment	Page no
DIGITAL DESIGN FLOW		
1	An inverter	3-4
2	Buffer	5-6
3	Transmission Gate	7-8
4	Basic Gates	9-13
5a	D-Flip-flop	14-16
5b	JK-Flip-flop	17-19
5c	Master Slave JK Flip-flop	20-22
5d	SR-Flip-flop	23-25
5e	T-Flip-flop	26-27
6a	Serial Adder	29-30
6b	Parallel Adder	31-33
7	Asynchronous Counter	34-36
8	Synchronous Counter	37-39
ANALOG DESIGN FLOW		
1	An inverter	40-74
2a	Common Source Amplifier	76-80
2b	Common Drain Amplifier	81-86
2c	Differential Amplifier	87-106
3	Operational amplifier	107-112
4	R-2R DAC	113-117
5	VIVA QUESTIONS	118

Course outcomes:

On the completion of this laboratory course, the students will be able to:

- Write test bench to simulate various digital circuits.
- Interpret concepts of DC Analysis, AC Analysis and Transient Analysis in analog circuits.
- Design and simulate basic CMOS circuits like inverter, common source amplifier and differential amplifiers.
- Use basic amplifiers and further design higher level circuits like operational amplifier and analog/digital converters to meet desired parameters.
- Use transistors to design gates and further using gates realize shift registers and adders to meet desired parameters.

PART A: ASIC – Digital Design**PROCEDURE FOR CREATING DIGITAL SIMULATION USING VERILOG AND CADENCE DIGITAL TOOL**

Open Terminal Window and use the following commands

Procedure for Simulation:

1. Change directory to Cadence_Digital_labs/Workarea/Inverter using commands:

```
>cdh  
>source/cad/cshrc
```

2. Type the programs design code and testbench code using editor in workarea folder and save

Create the design file (Verilog module) using editor gedit

```
>gedit filename.v
```

The file name can be changed with respect to the experiments.

Create the testbench file (Verilog module) using editor gedit

```
>gedit tb_filename.v
```

The testbench file name can be changed with respect to the design file.

3. Compile the source Descriptions: (i) Compile the Inverter description with the -messages option:

```
>ncvlog -mess (name of the file) (name of the testbench file)
```

Example:

```
>ncvlog -mess inv.v inv_tb
```

Note: Check out for error and warnings. If any, then go back to text editor and edit and the compile

4. Elaborate the top level Design using the command:

>ncelab -mess -access +rwc (name of the testbench file without file type)

Example: >ncelab -mess -access+rwc inv_tb //Do not include file type for testbench file

5. Simulate the Top-Level Design in Non GUI mode

>ncsim -mess -gui (name of the testbench file)

Now a console and Design Browser windows of Simvision are opened and click on the waveform button in the toolbar to send the selected objects to waveform window.

Waveform Window opens and Press run to run the simulation for a time period specified in the time field.

Procedure for Synthesis using Cadence Tool

The Verilog code, technology library and the constraint files are input to the logical synthesis. The tool will generate the gate level netlist and gives the output as: gatelevel schematic and the report of area, power and timing.

6. Create a file named Constraints_sdc.sdc

The timing constraints are defined in this file. Example of one such file is as shown –

```
create_clock -name clk -period 10 -waveform {0 5} [get_ports "clk"]
set_clock_transition -rise 0.1 [get_clocks "clk"]
set_clock_transition -fall 0.1 [get_clocks "clk"]
set_clock_uncertainty 1.0 [get_ports "clk"]
set_input_delay -max 1.0 [get_ports "A"] -clock [get_clocks "clk"]
set_input_delay -max 1.0 [get_ports "B"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "sum"] -clock [get_clocks "clk"]
```

There are three different parts in the constraint file:

a. Clock definition and clock constraints –

Clock definition

```
create_clock -name clk -period 10 -waveform {0 5} [get_ports "clock"]
```

Clock rise time

```
set_clock_transition -rise 0.1 [get_clocks " clk "]
```

Clock fall time

```
set_clock_transition -fall 0.1 [get_clocks " clk "]
```

Uncertainties of Clock

```
set_clock_uncertainty 1.0 [get_ports " clk "]
```

b. Input port timing constraints –

```
set_input_delay -max 1.0 [get_ports " A"] -clock [get_clocks " clk "]
```

Input port delay

```
set_input_delay -max 1.0 [get_ports " B"] -clock [get_clocks " clk "]
```

Input port delay

c. Output port timing constraints –

Output port delay

```
set_output_delay -max 1.0 [get_ports " sum " ] -clock [get_clocks " clk "]
```

The port names that are used in the constraint file (bolded) must match with the names that are used in the Verilog program of the main design module. The constraints are defined for all the ports in the design.

7. Synthesis the top level design

The verilog file to be synthesized must be copied into this directory.

Copy rc folder that created for simulation in desktop into user directory.

Open the rc_script file in editor and change the file name to:

```
read_hdl {filename.v}    // filename.v is the Design code file
               {inv.v}      // for example inv.v as filename.v
```

```
>rc -f -gui rc_script.tcl
```

Script file contains the Verilog RTL code, standard library file for a particular technology,


1. Inverter

AIM: To write verilog code for an inverter circuit and its testbench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

The NOT gate or an inverter is an electronic circuit that produces an inverted version of the input at its output. It is also known as an inverter. If the input variable is A, the inverted output is known as NOT A. This is also shown as A', or A with a bar over the top, as shown at the outputs. The diagrams below show two ways that the NAND logic gate can be configured to produce a NOT gate. It can also be done using NOR logic gates in the same way.

 

NOT gate	
A	\bar{A}
0	1
1	0

PROGRAM:

```
/*Inverter program Verilog code-file name
inv.v */
```

```
module inv(i1,o1);
input i1;
output o1;
assign o1 = ~i1;
endmodule
```

```
/*Inverter program Verilog code for
testbench -file name tb_inv.v*/
```


```
module tb_inv;
reg i1;
wire o1;
inv dut_inv(i1,o1);
initial begin
i1 = 1'b0;
#5 i1 = 1'b1;
#5 i1 = 1'bX;
#5 i1 = 1'bZ;
end
endmodule
```

Constraints file for Synthesis:


```
set_input_delay -max 1.0 [get_ports "i1"]
set_output_delay -max 1.0 [get_ports "o1"]
```

OUTPUT:

Simulation:

 

Synthesis

 

RESULT: Verilog code for the inverter circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.


2. A Buffer

AIM: To write Verilog code for an buffer circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool


THEORY: A special logic gate called a buffer is manufactured to perform the same function as two inverters. Its symbol is simply a triangle, with no inverting “bubble” on the output terminal. Buffer gates merely serve the purpose of signal amplification: taking a “weak” signal source that isn’t capable of sourcing or sinking much current, and boosting the current capacity of the signal so as to be able to drive a load.

"Buffer" gate

 

Input	Output
0	0
1	1

Buffer Circuit

 

PROGRAM :

```
/*Buffer program Verilog code-file name
buffer.v*/
```



```
module buffer(x,y);
input x;
output y;
wire t1;
inv ins1(x,t1);
inv ins2(t1,y);
endmodule
```

```
/*Buffer program Verilog code for
testbench -file name tb_buffer.v*/
```

```
module tb_buffer;
reg x;
wire y;
buffer dut_buffer(x,y);
initial begin
x = 1'b0;
#5 x = 1'b1;
#5 x = 1'bX;
#5 x = 1'bZ;
end
endmodule
```

Constraints file for Synthesis:

```
set_input_delay -max 1.0 [get_ports "x"]
set_output_delay -max 1.0 [get_ports "y"]
```

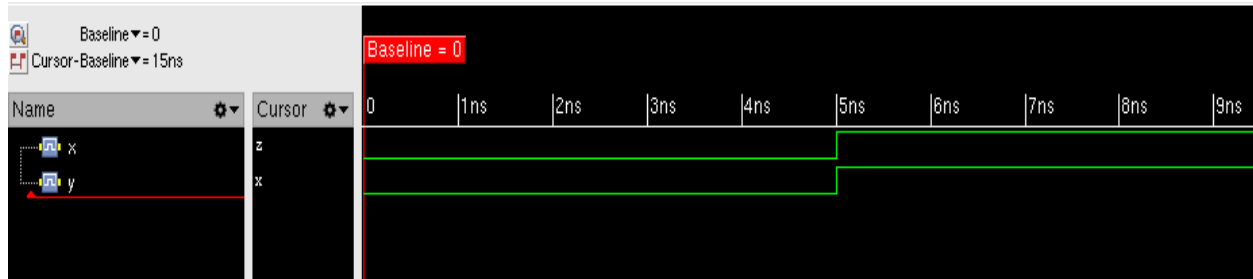 OUTPUT:**Simulation:****Synthesis:**

RESULT: Verilog code for the buffer circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.


3. Transmission Gate

AIM: To write verilog code for Transmission Gate circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool


THEORY: A transmission gate, or analog switch, is defined as an electronic element that will selectively block or pass a signal level from the input to the output. Basic Operation This solid-state switch is comprised of a pMOS transistor and nMOS transistor. The control gates are biased in a complementary manner so that both transistors are either on or off. When the voltage on node A is a Logic 1, the complementary Logic 0 is applied to node active-low A, allowing both transistors to conduct and pass the signal at IN to OUT. When the voltage on node active-low A is a Logic 0, the complementary Logic 1 is applied to node A, turning both transistors off and forcing a high-impedance condition on both the IN and OUT nodes. This high-impedance condition represents the third "state" (high, low, or high-Z) that the channel may reflect downstream. The schematic diagram (Figure 1) includes the arbitrary labels for IN and OUT, as the circuit will operate in an identical manner if those labels were reversed. This design provides true bidirectional connectivity without degradation of the input signal.

Symbol of Transmission Gate

 

Truth table of Transmission gate

Control	IN	OUT
0	X	0
1	0	0
1	1	1

 

PROGRAM:

```
/*transmission gate program Verilog code-
file name transgate.v*/
```



```
module transgate(x,cntrl,y);
input x,cntrl;
output y;
assign y = cntrl?x:1'bz;
endmodule
```

```
/*transmission gate program Verilog code
for testbench -file name tb_transgate.v*/
```

```
module tb_transgate;
reg x,cntrl;
wire y;
transgate dut_transgate(x,cntrl,y);
initial begin
x = 1'b0; cntrl = 1'b0;
#5 x = 1'b1; cntrl = 1'b1;
#5 x = 1'bx; cntrl = 1'b0;
#5 x = 1'bz; cntrl = 1'b1;
end
endmodule
```

Constraints file for Synthesis:

```
set_input_delay -max 1.0 [get_ports "x"]
set_input_delay -max 1.0 [get_ports "cntrl"]
set_output_delay -max 1.0 [get_ports "y"]
```

 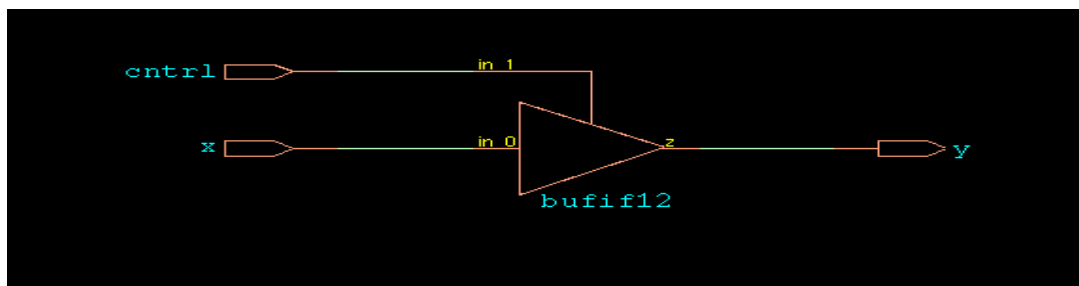OUTPUT:**Simulation:****Synthesis:**

RESULT: Verilog code for the transmission gate circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.

4. Basic Gates

AIM:


To write verilog code for an universal Gate circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:


Digital systems are said to be constructed by using logic gates. These gates are the AND, OR, NOT, NAND, NOR, EXOR and EXNOR gates.

1. AND gate

 


The AND gate is an electronic circuit that gives a **high** output (1) only if **all** its inputs are high. A dot (.) is used to show the AND operation i.e. A.B. Bear in mind that this dot is sometimes omitted i.e. AB

2. OR gate

 

The OR gate is an electronic circuit that gives a high output (1) if **one or more** of its inputs are high. A plus (+) is used to show the OR operation.


3. NOT gate

 

The NOT gate is an electronic circuit that produces an inverted version of the input at its output. It is also known as an *inverter*. If the input variable is A, the inverted output is known as NOT A. This is also shown


as A' , or A with a bar over the top, as shown at the outputs. The diagrams below show two ways that the NAND logic gate can be configured to produce a NOT gate. It can also be done using NOR logic gates in the same way.

4. EXOR gate

 


The 'Exclusive-OR' gate is a circuit which will give a high output if **either, but not both**, of its two inputs are high. An encircled plus sign (\oplus) is used to show the EXOR operation.

5. ENOR gate

 


The 'Exclusive-NOR' gate circuit does the opposite to the EXOR gate. It will give a low output if **either, but not both**, of its two inputs are high. The symbol is an EXOR gate with a small circle on the output. The small circle represents inversion.

6. NAND gate

 

 7. NOR GATE

A NOR gate is logically an inverted OR gate. It has the following truth table:



TRUTH TABLE

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

ProjectIoT123.com

Truth Table

A	B	NOT	AND	NAND	OR	NOR	EX-OR	EX-NOR
0	0	1	0	1	0	1	0	1
0	1	1	0	1	1	0	1	0
1	0	0	0	1	1	0	1	0
1	1	0	1	0	1	0	0	1

PROGRAM:

/*Basic gates program Verilog code-file name basicgates.v*/

```

module basicgates(i1,i2,sel,y);
input i1,i2;
input [2:0] sel;
output reg y;
always@(sel or i1 or i2)
begin
case (sel)
3'b000: y = ~i1;
3'b001: y = i1 & i2;
3'b010: y = i1 | i2;
3'b011: y = ~(i1 & i2);
3'b100: y = ~(i1 | i2);
3'b101: y = (i1 ^ i2);
3'b110: y = ~(i1 ^ i2);
3'b111: y = i2;
endcase
end
endmodule

```

/*Basic gates program Verilog code for testbench file name tb_basicgates.v*/



```

module tb_basicgates;
reg i1,i2;
reg [2:0] sel;
wire y;
basicgates dut_basicgates(i1,i2,sel,y);
initial begin
i1 = 1'b1 ; i2 = 1'b0;
sel = 3'b000;
#5 sel = 3'b001;
#5 sel = 3'b010;
#5 sel = 3'b011;
#5 sel = 3'b100;
#5 sel = 3'b101;
#5 sel = 3'b110;
#5 sel = 3'b111;
#5;
end
endmodule.

```

Constraints file for Synthesis:

```
set_input_delay -max 1.0 [get_ports "i1"]  
set_input_delay -max 1.0 [get_ports "i2"]  
set_input_delay -max 1.0 [get_ports "sel"]  
set_output_delay -max 1.0 [get_ports "y"]
```

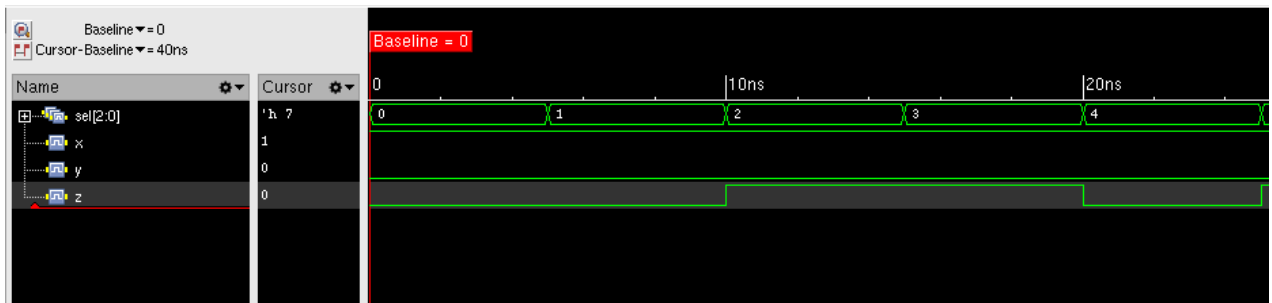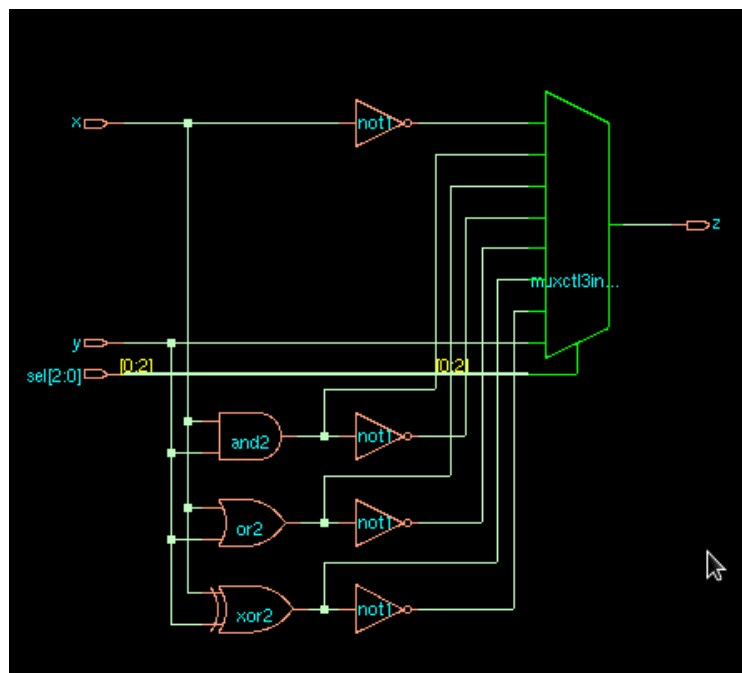OUTPUT:**Simulation:****Synthesis:**

RESULT: Verilog code for the all basic gates and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.


5a. D Flip-Flop

AIM: To write verilog code for an D flip-flop circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY: In electronics, a flip-flop or latch is a circuit that has two stable states and can be used to store state information. A flip-flop is a bistable multivibrator. The circuit can be made to change state by signals applied to one or more control inputs and will have one or two outputs. It is the basic storage element in sequential logic. Flip-flops and latches are fundamental building blocks of digital electronics systems used in computers, communications, and many other types of systems. Flip-flops and latches are used as data storage elements. A flip-flop stores a single bit (binary digit) of data; one of its two states represents a "one" and the other represents a "zero". Such data storage can be used for storage of state, and such a circuit is described as sequential logic.

 D flip-flop The D flip-flop is widely used. It is also known as a "data" flip-flop. The D flip-flop captures the value of the D-input at a definite portion of the clock cycle (such as the rising edge of the clock). That captured value becomes the Q output. At other times, the output Q does not change. The D flip-flop can be viewed as a memory cell, a zero-order hold, or a delay line.



D-FF SYMBOL

Truth Table

reset	clock	d	q	qb
0	↑	1	1	0
0	↑	0	0	1
0	0	X	X	Hold
1	↑	X	0	1

('X' denotes a **Don't care** condition, meaning the signal is irrelevant & **'Hold'** means output follows the previous state).

PROGRAM :

```
/*D Flip-flop program Verilog code-file name
dff.v*/
```

```
module dff(clk,rst,din,q,qb);
input clk,rst,din;
output q,qb;
reg q;
assign qb = ~q;
always@(posedgeclk)
begin
if(rst)
q<= 1'b0;
else
q<=din;
end
endmodule
```

```
/*D flip-flop program Verilog code for
testbench -file name tb_dff.v*/
```


```
module tb_dff;
reg clk,rst;
reg ndin;
wire q,qb;
dff dut_dff(clk,rst,din,q,qb);
initial begin /* generating the clock
stimulus */
clk = 1'b0;
forever #5 clk = ~clk;
end
initial begin /* generating the flop input
stimulus */
rst = 1'b1;
#20 rst = 1'b0;
#20 din = 1'b0;
#20 din = 1'b1;
#200 $finish;
end
endmodule
```

Constraints file for Synthesis:


```
create_clock -name clk -period 10 -waveform {0 5} [get_ports "clk"]
set_clock_transition -rise 0.1 [get_clocks "clk"]
set_clock_transition -fall 0.1 [get_clocks "clk"]
set_clock_uncertainty 1.0 [get_ports "clk"]
set_input_delay -max 1.0 [get_ports "rst"] -clock [get_clocks "clk"]
set_input_delay -max 1.0 [get_ports "din"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "q"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "qb"] -clock [get_clocks "clk"]
```


OUTPUT

Simulation:

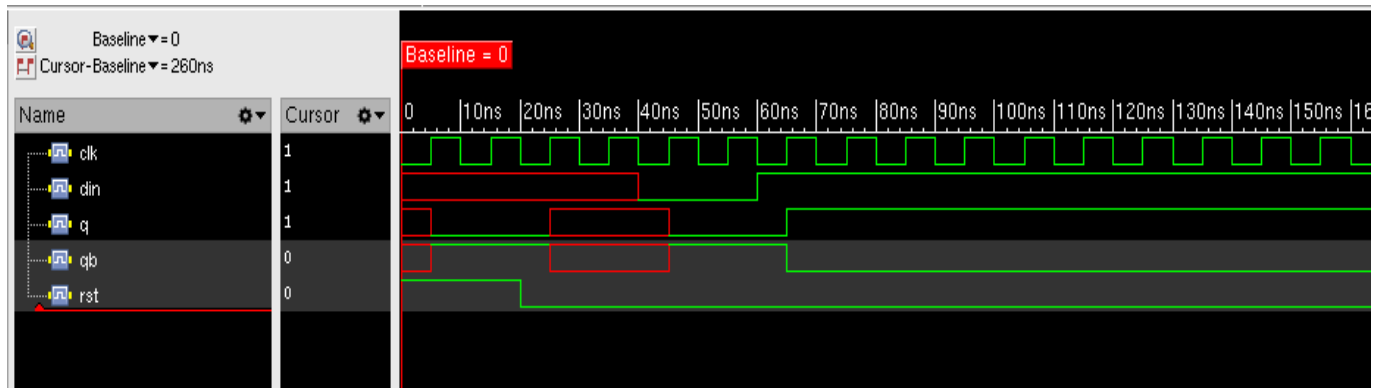

Synthesis:

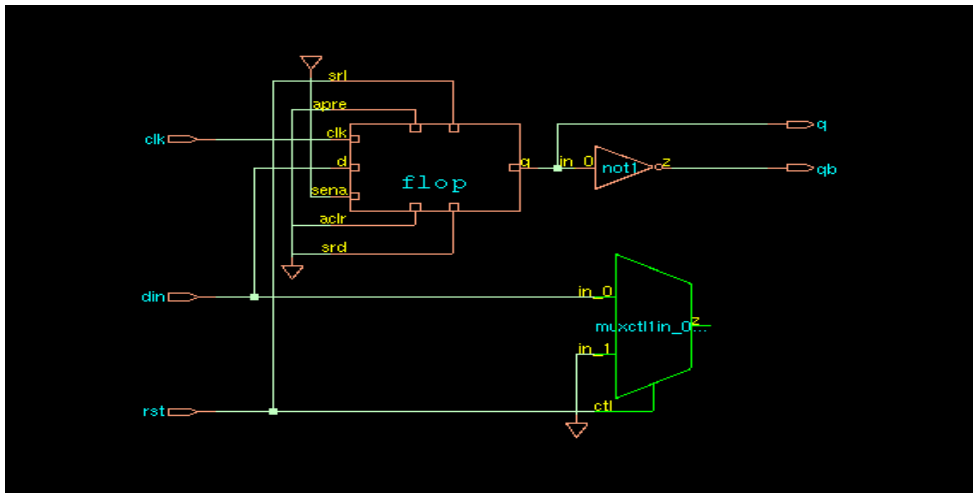

RESULT: Verilog code for the D flip-flop circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.

5b. JK Flip-Flop


AIM: To write verilog code for an JK flip-flop circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

Then the JK flip-flop is basically an SR flip-flop with feedback which enables only one of its two input terminals, either SET or RESET to be active at any one time thereby eliminating the invalid condition seen previously in the SR flip-flop circuit. Also when both the J and the K inputs are at logic level “1” at the same time, and the clock input is pulsed either “HIGH”, the circuit will “toggle” from its SET state to a RESET state, or visa-versa. This result in the JK flip-flop acting more like a T-type toggle flip-flop when both terminals are “HIGH”

Although this circuit is an improvement on the clocked SR flip-flop it still suffers from timing problems called “race” if the output Q changes state before the timing pulse of the clock input has time to go “OFF”. To avoid this the timing pulse period (T) must be kept as short as possible (high frequency). As this is sometimes not possible with modern TTL IC’s the much improved MasterSlave JK Flip-flop was developed.

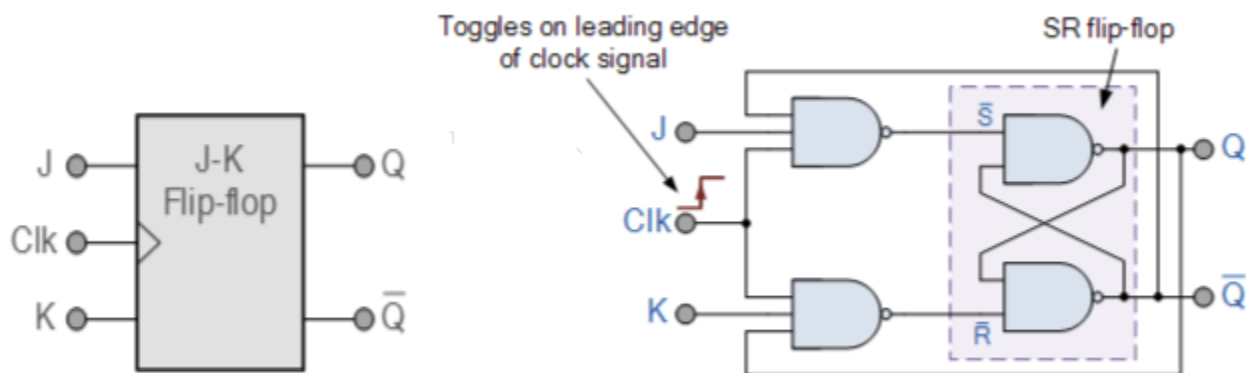

logic symbol

Circuit Diagram

Truth Table:

	Clk	J	K	Q	Qb	Comments
	↑	0	0	Hold		No change
Same as for SR latch	↑	0	1	0	1	Reset Q>>0
	↑	1	0	1	0	Set Q>>1
Toggle action	↑	1	1	0	1	Toggle
				1	0	

PROGRAM:



<pre> /*JK Flip-flop program Verilog code-file name jkff.v*/ module jkff(j,k,rst,clk,q,qb); input j,k,clk,rst; output q,qb; reg q; assign qb = ~q; always@(posedgeclk) begin if(rst) q <= 1'b0; else begin case ({j,k}) 2'b00: q <= q; 2'b01: q <= 1'b0; 2'b10: q <= 1'b1; 2'b11: q <= ~q; /*according to the definition of JK flip-flop*/ endcase end end endmodule </pre>	<pre> /*JK Flip-flop program Verilog code for testbench -file name tb_jkff.v*/ module tb_jkff; reg clk,rst; reg j,k; wire q,qb; jkff dut_jkff(j,k,rst,clk,q,qb); initial begin /* generating the clock stimulus*/ clk = 1'b0; forever #5 clk = ~clk; end initial begin /* generating the flop input stimulus*/ rst = 1'b1; #20 rst = 1'b0; #20 j = 1'b0 ; k = 1'b0; #20 j = 1'b0 ; k = 1'b1; #20 j = 1'b1 ; k = 1'b0; #20 j = 1'b1 ; k = 1'b1; #200 \$finish; end endmodule </pre>
---	--

Constraints file for Synthesis:

```

create_clock -name clk -period 10 -waveform {0 5} [get_ports "clk"]
set_clock_transition -rise 0.1 [get_clocks "clk"]
set_clock_transition -fall 0.1 [get_clocks "clk"]
set_clock_uncertainty 1.0 [get_ports "clk"]
set_input_delay -max 1.0 [get_ports "rst"] -clock [get_clocks "clk"]
set_input_delay -max 1.0 [get_ports "j"] -clock [get_clocks "clk"]
set_input_delay -max 1.0 [get_ports "k"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "q"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "qb"] -clock [get_clocks "clk"]

```

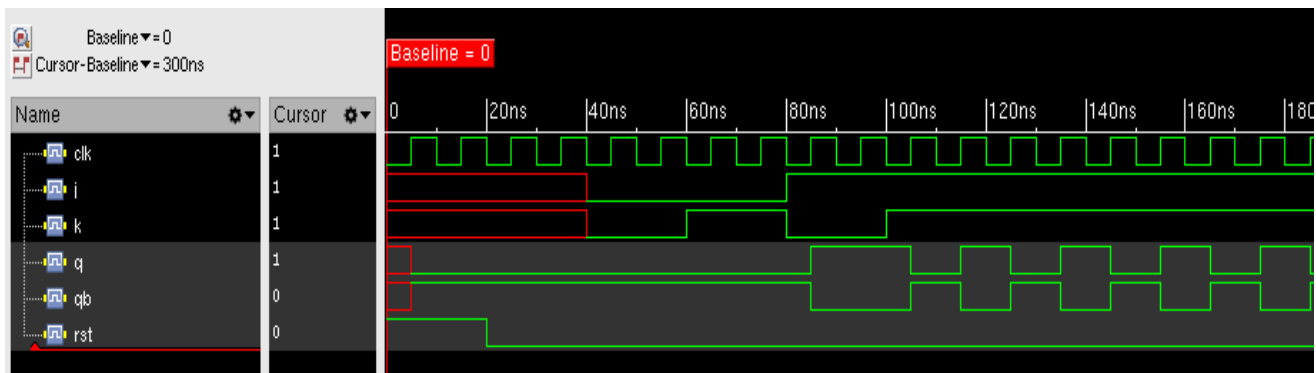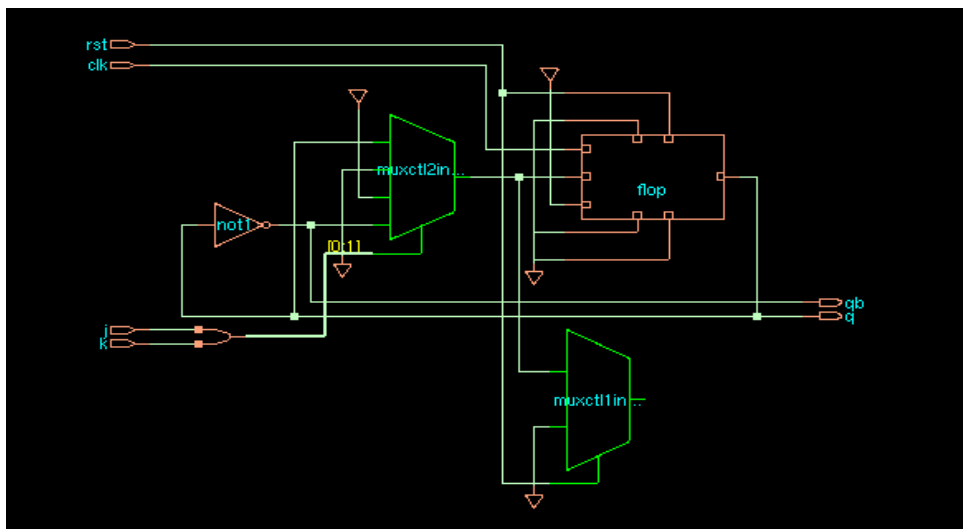OUTPUT:**Simulation:****Synthesis:****RESULT:**

Verilog code for the JK flip-flop circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.

5c. MASTER SLAVE JK Flip-Flop


AIM: To write verilog code for an MASTER SLAVE JK flip-flop circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

Master slave JK FF is a cascade of two S-R FF with feedback from the output of second to input of first. Master is a positive level triggered. But due to the presence of the inverter in the clock line, the slave will respond to the negative level. Hence when the clock = 1 (positive level) the master is active and the slave is inactive. Whereas when clock = 0 (low level) the slave is active and master is inactive.

Circuit Diagram

 

Truth Table

Inputs			Outputs		Comments
E	J	K	Q_{n+1}	\overline{Q}_{n+1}	
1	0	0	Q_n	\overline{Q}_n	No change
1	0	1	0	1	Rset
1	1	0	1	0	Set
1	1	1	\overline{Q}_n	Q_n	Toggle


PROGRAM:


```
/*Master – slave JK Flip-flop program
Verilog code-file name ms_jkff.v*/
```

```
module ms_jkff(j,k,rst,clk,qs,qsb,qm,qmb);
input j,k,clk,rst;
output qs,qsb,qm,qmb;
wire clkbar;
assign clkbar = ~clk;
jkff jk1(qm,qmb,j,k,clk,rst);
jkff jk1(qs,qsb,qm,qmb,clkbar,rst);
endmodule
```

```
/*Master – Slave JK Flip-flop program
Verilog code for testbench -file name
tb_msjkff.v*/
```

```
module tb_msjkff;
reg j,k,clk,rst;
wire qs,qsb,qm,qmb;
ms_jkff ms1(j,k,rst,clk,qs,qsb,qm,qmb);
initial
clk=1'b0;
always
#10 clk=~clk;
initial
begin
rst=1'b1; j=1'b0; k=1'b0;
#15 rst=1'b0;
#25 k=1'b1; j=1'b0;
#25 j=1'b1; k=1'b0;
#25 k=1'b1; j=1'b1;
#200 $finish;
End
endmodule
```

 OUTPUT:**Simulation:**

 Synthesis:

RESULT: Verilog code for the master slave JK flip-flop circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.


5d. SR Flip-Flop

AIM: To write verilog code for an SR flip-flop circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

It can be seen that when both inputs $S = "1"$ and $R = "1"$ the outputs Q and \bar{Q} can be at either logic level "1" or "0", depending upon the state of the inputs S or R BEFORE this input condition existed. Therefore the condition of $S = R = "1"$ does not change the state of the outputs Q and \bar{Q} . However, the input state of $S = "0"$ and $R = "0"$ is an undesirable or invalid condition and must be avoided. The condition of $S = R = "0"$ causes both outputs Q and \bar{Q} to be HIGH together at logic level "1" when we would normally want Q to be the inverse of \bar{Q} . The result is that the flip-flop loses control of Q and \bar{Q} , and if the two inputs are now switched "HIGH" again after this condition to logic "1", the flip-flop becomes unstable and switches to an unknown data state based upon the unbalance.

 

Truth Table

Clk	R	S	Q	Qb	comments
↑	0	0	Hold		No change
↑	0	1	1	0	set
↑	1	0	0	1	reset
↑	1	1	z	z	indeterminate
0	x	x	Hold		No change

PROGRAM:

```
/*SR Flip-flop program Verilog code-file
name srff.v*/
```



```
module srff(s,r,clk,rst,q,qb);
input clk,rst;
input s,r;
output q,qb;
reg q; /* always declare "q" as register
before you use it inside always block */
assign qb = ~q;
always@(posedgeclk)
begin
if(rst)
q <= 1'b0;
else
begin
case ({s,r})
2'b00: q <= q;
2'b01: q <= 1'b0;
2'b10: q <= 1'b1;
2'b11: q <= 1'bx;
endcase
end
end
endmodule
```

```
/*SR Flip-flop program Verilog code for
testbench-file name tb_srff.v*/
```

```
module tb_srff;
reg clk,rst;
reg s,r;
wire q,qb;
srff dut_srff(s,r,clk,rst,q,qb);
initial begin /*generating the clock stimulus*/
clk = 1'b0;
forever #5 clk = ~clk;
end
initial begin /*generating the flop input
stimulus*/
rst = 1'b1;
#20 rst = 1'b0;
#20 s = 1'b0 ; r = 1'b0;
#20 s = 1'b0 ; r = 1'b1;
#20 s = 1'b1 ; r = 1'b0;
#20 s = 1'b1 ; r = 1'b1;
#200 $finish;
end
endmodule
```

Constraints file for Synthesis:

```
create_clock -name clk -period 10 -waveform {0 5} [get_ports "clk"]
set_clock_transition -rise 0.1 [get_clocks "clk"]
set_clock_transition -fall 0.1 [get_clocks "clk"]
set_clock_uncertainty 1.0 [get_ports "clk"]
set_input_delay -max 1.0 [get_ports "rst"] -clock [get_clocks "clk"]
set_input_delay -max 1.0 [get_ports "s"] -clock [get_clocks "clk"]
set_input_delay -max 1.0 [get_ports "r"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "q"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "qb"] -clock [get_clocks "clk"]
```

 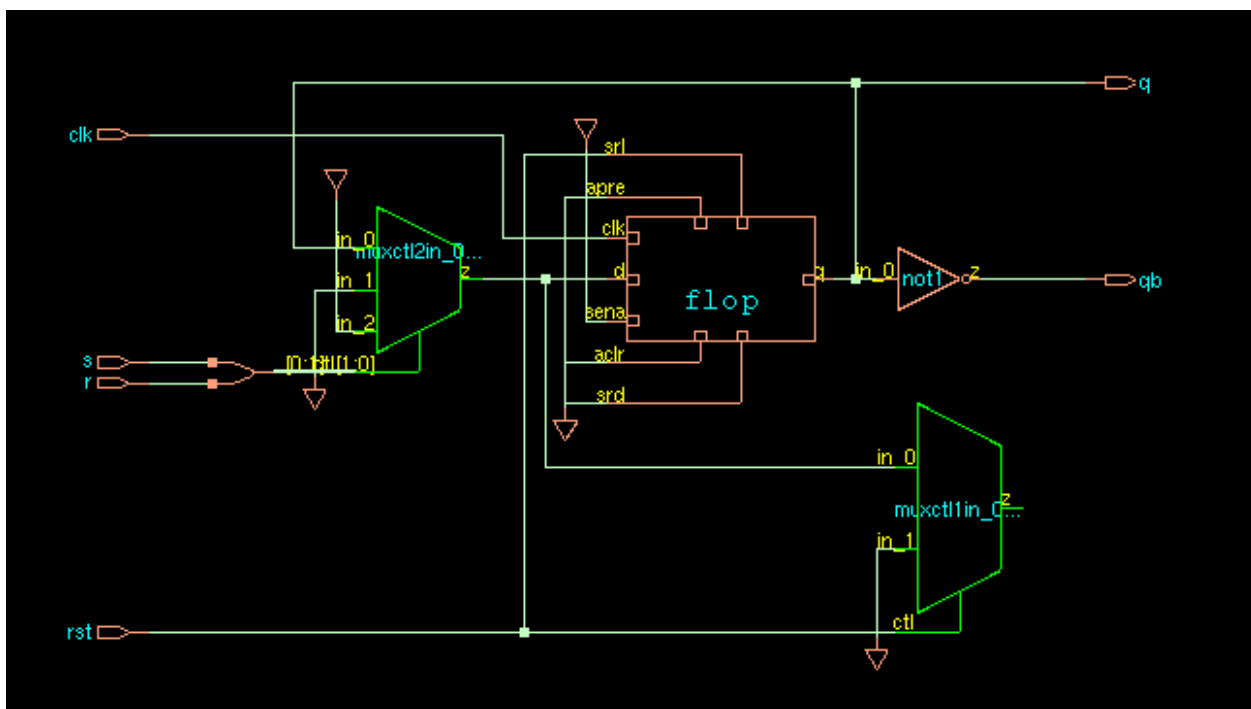OUTPUT:**Simulation:****Synthesis:**

RESULT: Verilog code for the SR flip-flop circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.

5e. T Flip-Flop


AIM: To write verilog code for an T flip-flop circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

A circuit symbol for a T-type flip-flop. If the T input is high, the T flip-flop changes state ("toggles") whenever the clock input is strobed. If the T input is low, the flip-flop holds the previous value. This behavior is described by the truth table.

When T is held high, the toggle flip-flop divides the clock frequency by two; that is, if clock frequency is 4 MHz, the output frequency obtained from the flip-flop will be 2 MHz. This "divide by" feature has application in various types of digital counters. A T flip-flop can also be built using a JK flip-flop (J & K pins are connected together and act as T) or a D flip-flop (T input XOR Previous drives the D input).

 

Logic symbol

Truth Table

Reset	Clock	T	Q_{n-1}	Q	Q_b
0	↑	0	0	0	1
0	↑	0	1	1	0
0	↑	1	0	1	0
0	↑	1	1	0	1
1	↑	x	x	0	1

PROGRAM:

/*T Flip-flop program Verilog code-file name tff.v*/

```
module tff(clk,rst,T,q,qb);
input clk,rst,T;
output q,qb;
reg q;
assign qb = ~q;
always@(posedgeclk)
begin
if(rst)
q<= 1'b0;
else if(T)
q<=~q;
else
q<=q;
end
endmodule
```

/*T Flip-flop program Verilog code for testbench-file name tb_tff.v*/

```
module tb_tff;
reg clk,rst;
reg T;
wire nq,qb;
tff dut_tff(clk,rst,T,q,qb);
initial begin /* generating the clock stimulus */
clk = 1'b0;
forever #5 clk = ~clk;
end
initial begin /* generating the flop input stimulus */
rst = 1'b1;
#20 rst = 1'b0;
#20 T = 1'b0;
#20 T = 1'b1;
```


```
#200 $finish;
end
endmodule
```


Constraints file for Synthesis:

```
create_clock -name clk -period 10 -waveform {0 5} [get_ports "clk"]
set_clock_transition -rise 0.1 [get_clocks "clk"]
set_clock_transition -fall 0.1 [get_clocks "clk"]
set_clock_uncertainty 1.0 [get_ports "clk"]
set_input_delay -max 1.0 [get_ports "rst"] -clock [get_clocks "clk"]
set_input_delay -max 1.0 [get_ports "T"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "q"] -clock [get_clocks "clk"]
set_output_delay -max 1.0 [get_ports "qb"] -clock [get_clocks "clk"]
```

OUTPUT:

Simulation:

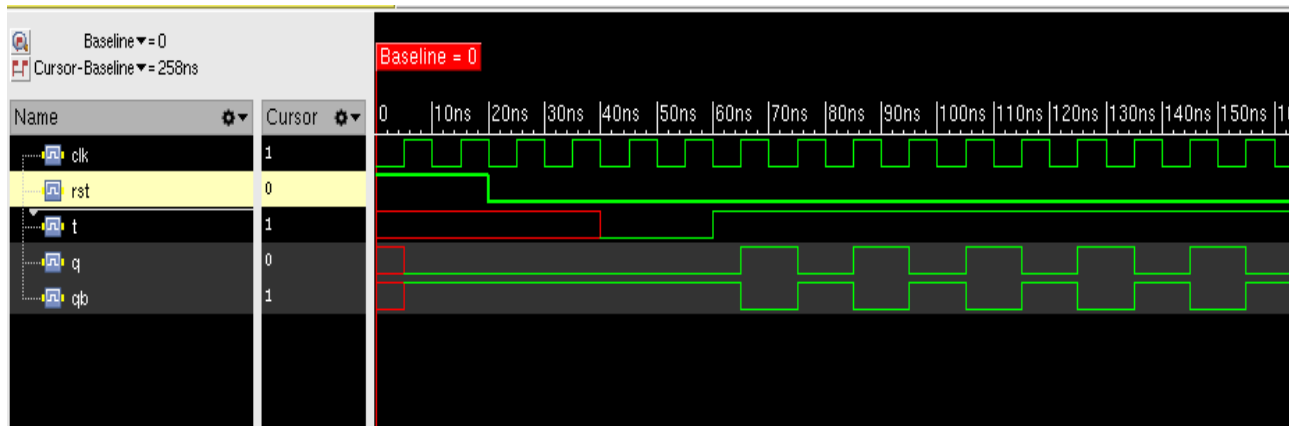

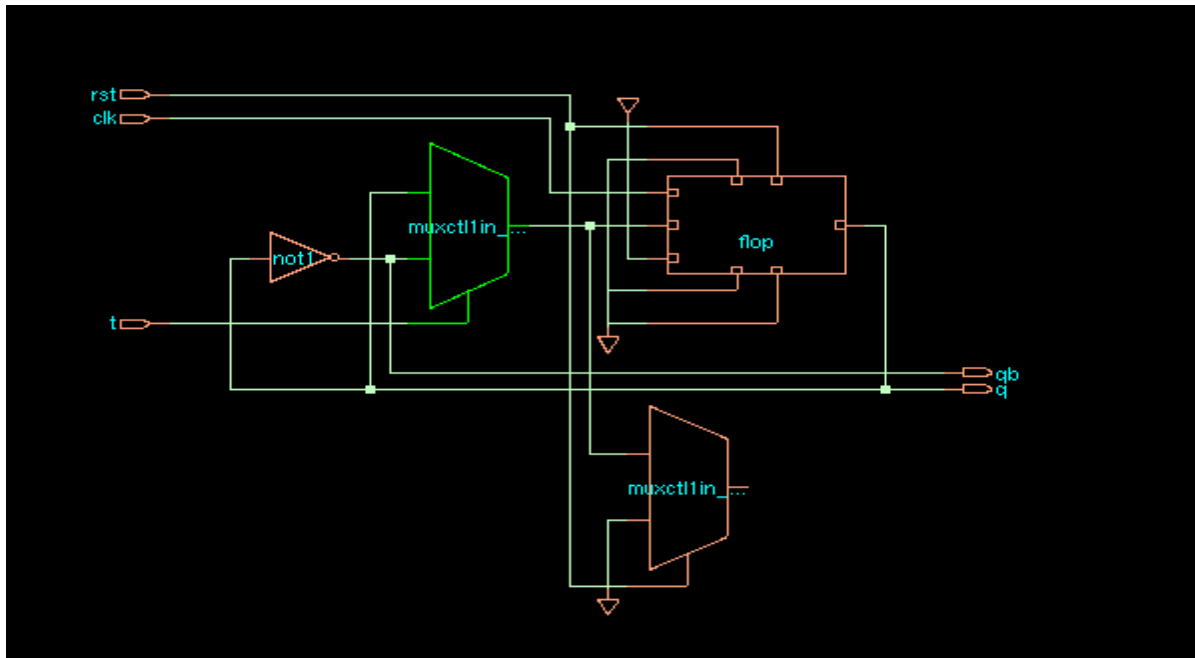Synthesis:

RESULT: Verilog code for the T flip-flop circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.


6a. Serial Adder

AIM: To write verilog code for Serial adder circuit and its testbench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

Serial adder is implemented using a 1 bit full adder. In this adder, there is a serial computation of inputs i.e. only single least significant bit (LSB) is taken as input to the 1 bit full adder along with the carry bit of previous computation and sum and carry out (Cout) is obtained for that bit position. Similarly the same process is carried out by shifting the input bits towards right and then all the 8-bits of both the input signals are computed along with all the carry outs generated and the sum is stored.

 

Truth Table

A	B	C	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

PROGRAM:



**/*Serial Adder program Verilog code-file
serialadder.v*/**

```
//Verilog code
module serial_adder(clk,rst,A,B,FSUM);
input [7:0] A,B;
input clk, rst;
output [8:0] FSUM;
reg [3:0] i;
reg [8:0] c;
reg [7:0] sum;
assign FSUM = {c[8],sum[7:0]};

always@(posedge clk)
begin
if(rst)
begin
c[0] <= 1'b0;
i <= 4'd0;
end
else
begin
sum[i] <= A[i]^B[i]^C[i];
C[i+1] <= A[i]&B[i] | B[i]&C[i] & C[i]&A[i];
i <= i+1;
end
end
endmodule
```

**/*Full Adder program Verilog code for Test
bench-file name tb_serial_adder.v*/**

```
module tb_serial_adder;
reg [7:0] A,B;
reg clk,rst;
wire [8:0] FSUM;
serial_adder dut_serial_adder(clk,
rst,A,B,FSUM);
initial begin
clk=1'b0;
forever #5 clk=~clk;
end
initial begin
rst=1'b1;
#20 rst = 1'b0;
A = 8'd124;
B = 8'd242;
#100 rst = 1'b1;
#20 rst = 1'b0;
A = 8'd200;
B = 8'd196;
#140 $finish;
end
endmodule
```

  OUTPUT:**Simulation:****Synthesis:**

RESULT: Verilog code for the serial adder circuit and its test bench for verification written, the waveform is observed and the code is synthesized with the technological library and is verified.


6b. Parallel Addder

AIM: To write verilog code for an parallel adder circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

Addition is a fundamental operation for any digital system, digital signal processing or control system. A fast and accurate operation of a digital system is greatly influenced by the performance of the resident adders. Adders are also very important component in digital systems because of their extensive use in other basic digital operations such as subtraction, multiplication and division. Parallel adder is a combinatorial circuit (not clocked, does not have any memory and feedback) adding every bit position of the operands in the same time. Thus it is requiring number of bit-adders (full adders + 1 half adder) equal to the number of bits to be added. The Parallel adder is constructed by cascading full adders (FA) blocks in series. One full adder is responsible for the addition of two binary digits at any stage of the ripple carry. The carryout of one stage is fed directly to the carry-in of the next stage.

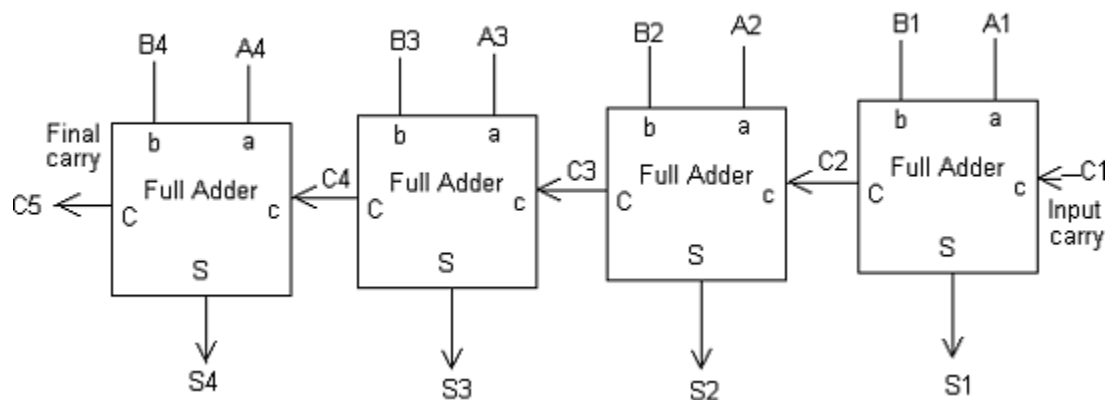

PROGRAM:

/*Parallel Addder program Verilog code-file name parallel_adder.v*/

```
module parallel_adder(in1,in2,fsum);
input [3:0] in1,in2;
output [4:0] fsum; /* this is 5 bit because we are
considering the final carryout(1 bit) also along with
the sum (4bit)*/
wire [2:0] tc; /* this is for the intermediate carry
that gets generated for the parallel adder*/
wire cin; /* initial carry input*/
```



/*Parallel Addder program Verilog code for test bench-file name tb_parallel_adder.v*/

```
module tb_parallel_adder;
reg [3:0] in1,in2;
wire [4:0] fsum;
parallel_adder
dut_parallel_adder(in1,in2,fsum);
initial begin
in1 = 4'b0000; in2 = 4'b0101;
#10 in1 = 4'b1000; in2 = 4'b0101;
#10 in1 = 4'b0100; in2 = 4'b0101;
```

```

assign cin = 1'b0; /* for a 4 bit parallel adder cin is
always 0 */
fulladder FA1(in1[0],in2[0],cin,fsum[0],tc[0]);
fulladder FA2(in1[1],in2[1],tc[0],fsum[1],tc[1]);
fulladder FA3(in1[2],in2[2],tc[1],fsum[2],tc[2]);
fulladder FA4(in1[3],in2[3],tc[2],fsum[3],fsum[4]);
endmodule
#10 in1 = 4'b0000; in2 = 4'b1101;
#10 in1 = 4'b0110; in2 = 4'b0101;
#10 in1 = 4'b1000; in2 = 4'b0111;
#30;
end
endmodule

```

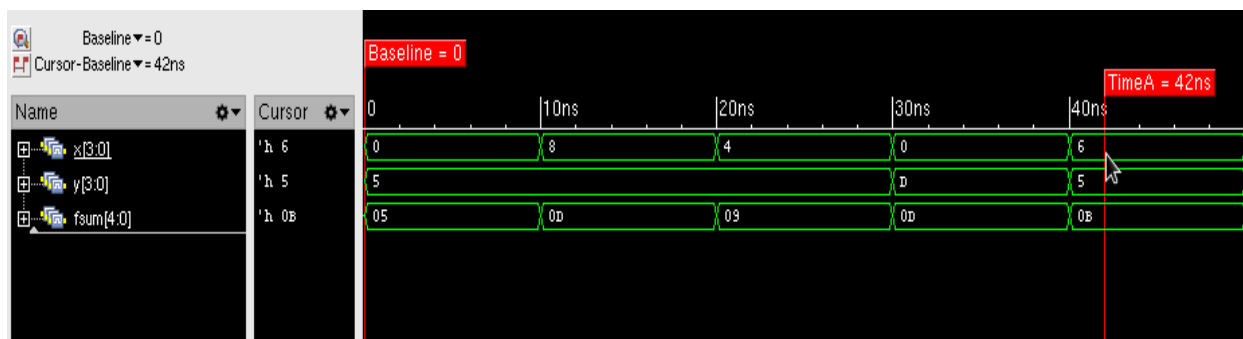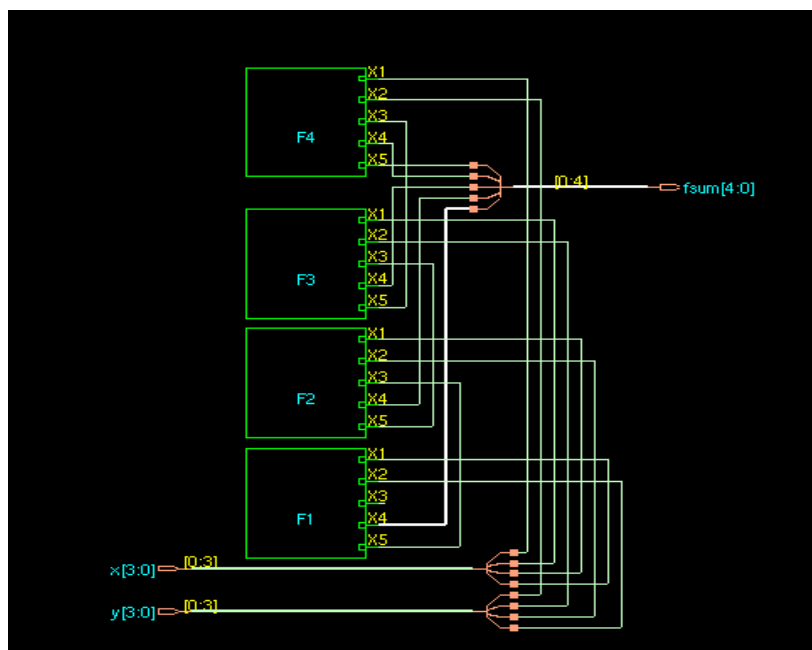OUTPUT:**Simulation:****Synthesis:**

RESULT: Verilog code for the parallel adder circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.

7. Asynchronous counter

AIM: To write Verilog code for asynchronous counter circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.


TOOL REQUIRED: Cadence Tool


THEORY:

A ripple counter is an asynchronous counter where only the first flip-flop is clocked by an external clock. All subsequent flip-flops are clocked by the output of the preceding flip-flop. Asynchronous counters are also called ripple-counters because of the way the clock pulse ripples it way through the flip-flops.

The MOD of the ripple counter or asynchronous counter is 2^n if n flip-flops are used. For a 4-bit counter, the range of the count is 0000 to 1111 (24 - 1). A counter may count up or count down or count up and down depending on the input control. The count sequence usually repeats itself. When counting up, the count sequence goes from 0000, 0001, 0010, ... 1110, 1111, 0000, 0001, ... etc. When counting down the count sequence goes in the opposite manner: 1111, 1110, ... 0010, 0001, 0000, 1111, 1110, ... etc. Four J-K flip-flops connected in such a way to always be in the “toggle” mode, we need to determine how to connect the clock inputs in such a way so that each succeeding bit toggles when the bit before it transitions from 1 to 0. The Q outputs of each flip-flop will serve as the respective binary bits of the final, four-bit count. If we used flip-flops with negative-edge triggering (bubble symbols on the clock inputs), we could simply connect the clock input of each flip-flop to the Q output of the flip-flop before it, so that when the bit before it changes from a 1 to a 0, the “falling edge” of that signal would “clock” the next flip-flop to toggle the next bit.

A four-bit “up” counter

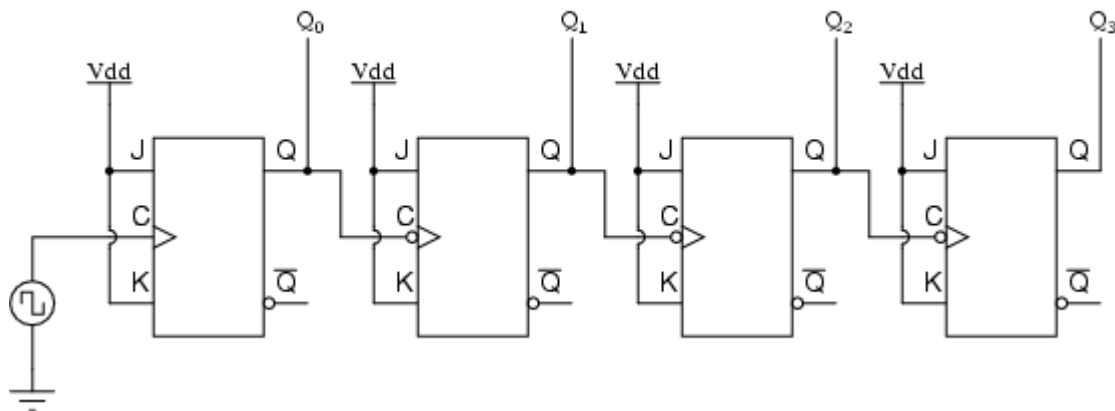

 **PROGRAM:**

```
/*Asynchronous counter program
Verilog code-file nameasynchcounter.v*/
```

```
module asynccounter(clk,rst,cout);
input clk,rst;
output [3:0] cout;
reg [3:0] cout;
always@(posedgeclk or negedge rst)
begin
if(!rst) /* we are considering active_low
rst*/
cout<=4'd0;
else
cout<= cout+1;
end
endmodule
```

```
/*Asynchronous counter program Verilog
code for testbench-file
nametb_asynccounter.v*/
```

```
module tb_asynccounter;
reg clk,rst;
wire [3:0] cout;
asynccounter dut_asynccounter(clk,rst,cout);
initial begin /* generating the clock stimulus
*/
clk = 1'b0;
forever #5 clk = ~clk;
end
initial begin
rst = 1'b0;
#20 rst = 1'b1;
#80 rst = 1'b0; /* this stimulus is to show that
this is a asynchronous reset and so we can
reset it in between the clock */
#5 rst = 1'b1 ;/* we will see in the simulation
that this reset will be recognised by the
design irrespective to what the clock status is
, thus making it a asynchronous design*/
#500 $finish;
end
endmodule
```

Simulation:

8. Synchronous Counter


AIM: To write verilog code for synchronous counter circuit and its test bench for verification, observe the waveform and synthesize the code with technological library with given Constraints.

TOOL REQUIRED: Cadence Tool

THEORY:

A synchronous counter, in contrast to an asynchronous counter, is one whose output bits change state simultaneously, with no ripple. The only way we can build such a counter circuit from J-K flip-flops is to connect all the clock inputs together, so that each and every flip-flop receives the exact same clock pulse at the exact same time. The figure shows a four-bit synchronous “up” counter. Each of the higher-order flip-flops are made ready to toggle (both J and K inputs “high”) if the Q outputs of all previous flip-flops are “high.” Otherwise, the J and K inputs for that flip-flop will both be “low,” placing it into the “latch” mode where it will maintain its present output state at the next clock pulse. Since the first (LSB) flip-flop needs to toggle at every clock pulse, its J and K inputs are connected to Vcc or Vdd, where they will be “high” all the time. The next flip-flop need only “recognize” that the first flip-flop’s Q output is high to be made ready to toggle, so no AND gate is needed. However, the remaining flip-flops should be made ready to toggle only when all lower-order output bits are “high,” thus the need for AND gates.

A four-bit synchronous “up” counter

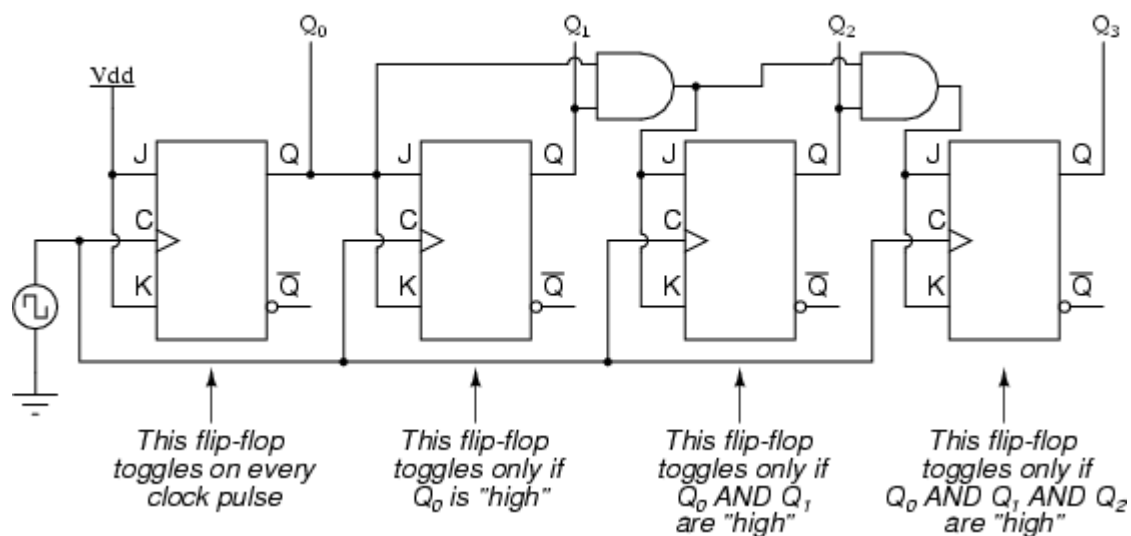


PROGRAM:


```
/*Synchronous counter program
Verilog code-file name
Synccounter.v*/
```

```
module synccounter(clk,rst,cout);
input clk,rst;
output [3:0] cout;
reg [3:0] cout;
always@(posedgeclk)
begin
if(!rst) /* we are considering
active_lowrst*/
cout<=4'd0;
else
cout<= cout+1;
end
endmodule
```

```
/*Synchronous counter program Verilog
code for test bench-file name
tb_synccounter.v*/
```

```
module tb_synccounter;
reg clk,rst;
wire [3:0] cout;
synccounter dut_synccounter(clk,rst,cout);
initial begin /*generating the clock stimulus */
clk = 1'b0;
forever #5 clk = ~clk;
end
initial begin
rst = 1'b0;
#20 rst = 1'b1;
#80 rst = 1'b0; /* this stimulus is to show that
this is synchronous reset and so we cannot reset
it in between the clock */
#5 rst = 1'b1 ;/* we will see in the simulation
that this reset will not be recognized by the
design thus making it a synchronous design*/
#500 $finish;
end
endmodule
```

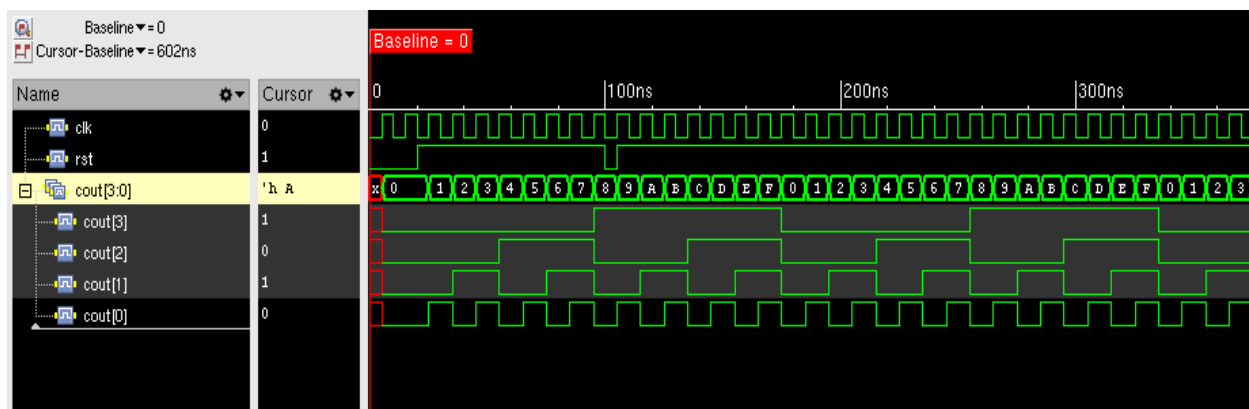OUTPUT:**Simulation:**

 Synthesis:

RESULT: Verilog code for the synchronous counter circuit and its test bench for verification is written, the waveform is observed and the code is synthesized with the technological library and is verified.


9 Successive Approximation Register

Aim: To compile and to simulate the Verilog code for the successive approximation Register.

Program

/*SAR program Verilog code-file name SAR.v*/	/*SAR program Verilog code for test bench-file name tb_SAR.v*/
<pre> module sar (digitalout,done,comp,start,reset,clk); output [3:0] digitalout; output done; input clk, start, reset, comp; reg [3:0]ring_count; reg [3:0]digital; wire D4,set0,set1,set2,set3; assign D4 = ring_count[0]; assign done = !D4; always @(posedge clk or negedge reset) begin if (~reset) ring_count <= 4'b1000; else begin if (start) ring_count <= 4'b1000; else ring_count <= (ring_count>>1); end end assign set3 = ring_count[3]; assign set2 = ring_count[2]; assign set1 = ring_count[1]; assign set0 = ring_count[0]; always @(posedge clk or negedge reset) begin if(~reset) digital[3] <= 1'b1; else if(start) digital[3] <= 1'b1; else if(set3) digital[3] <= comp; end always @(posedge clk or negedge reset) </pre>	<pre> module sar_tb; reg clk,reset,start; reg [63:0] vref_d,vin_d; wire done, comp; wire [3:0] digitalout; real vref_real = 7.5; sar s1 (digitalout,done,comp,start,reset,clk); dac d1 (comp,digitalout,vref_d,vin_d,clk,start); initial begin clk = 1'b1; start = 1'b1; #4000 \$finish; end always #10 clk = ~clk; initial begin #1;reset = 1'b1; #10; reset = 1'b0; #1; reset = 1'b1; end initial begin #10 ; stimulus (0.0,0.5,vref_real,8'd5); end task stimulus (input analog, input step, input reference, input [7:0]delay); real analog,step; real reference; begin while(analog <= reference) begin repeat(delay) @(posedge clk); start <= 1'b0; vref_d = \$realtobits (reference); </pre>


<pre> begin if(~reset) digital[2] <= 1'b1; else if(start) digital[2] <= 1'b1; else if(set2) digital[2] <= comp; end always @(posedge clk or negedge reset) begin if(~reset) digital[1] <= 1'b1; else if(start) digital[1] <= 1'b1; else if(set1) digital[1] <= comp; end always @(posedge clk or negedge reset) begin if(~reset) digital[0] <= 1'b1; else if(start) digital[0] <= 1'b1; else if(set0) digital[0] <= comp; end assign digitalout = (digital) (ring_count); endmodule module dac (comp,sar_out,vref_d,vin_d,clk,start); output comp; input clk,start; input [3:0]sar_out; input [63:0]vref_d; input [63:0]vin_d; reg comp; real v_dac,vref,vin; always @ (vin_d or start) begin vref = \$bitstoreal(vref_d); vin = \$bitstoreal(vin_d); end always @* begin </pre>	<pre> vin_d = \$realtobits (analog); @(posedge done) analog = analog + step; @(posedge clk); start <= 1'b1; end end endtask endmodule </pre>
---	---

 


PART B - Analog Design Flow

Procedure


1. Open the terminal.

 

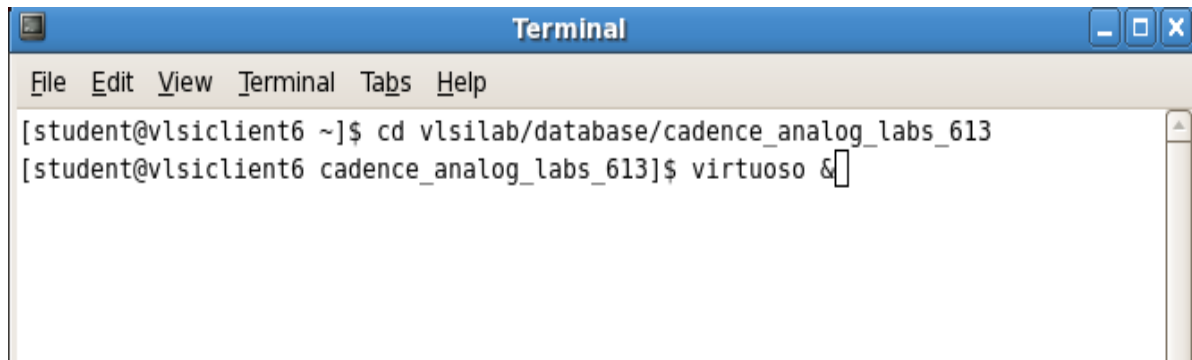
2. To invoke the tool, go to the specified directory where the tool is installed to. In the same terminal window, enter:
➤ **virtuoso&**



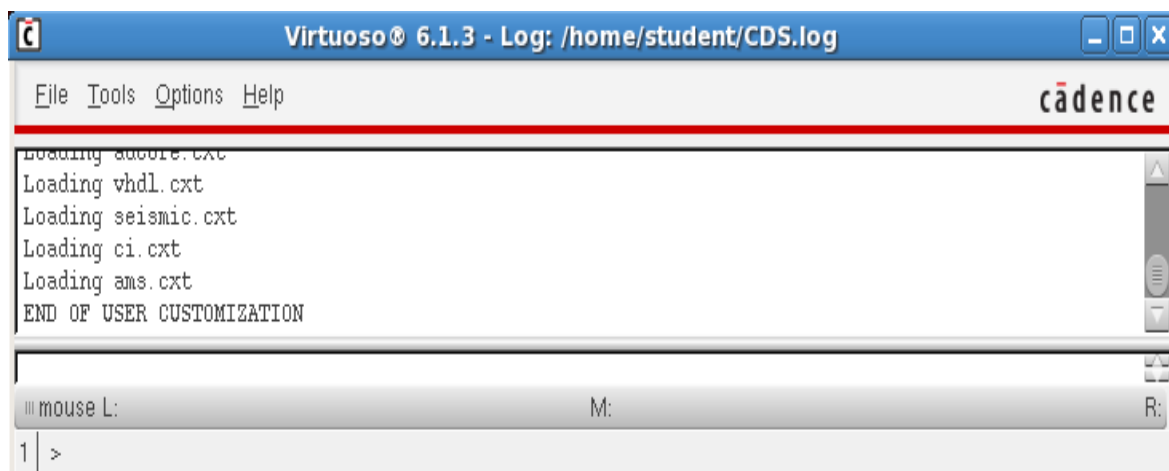The Virtuoso or Command Interpreter window(CIW) appears at the bottom of the screen



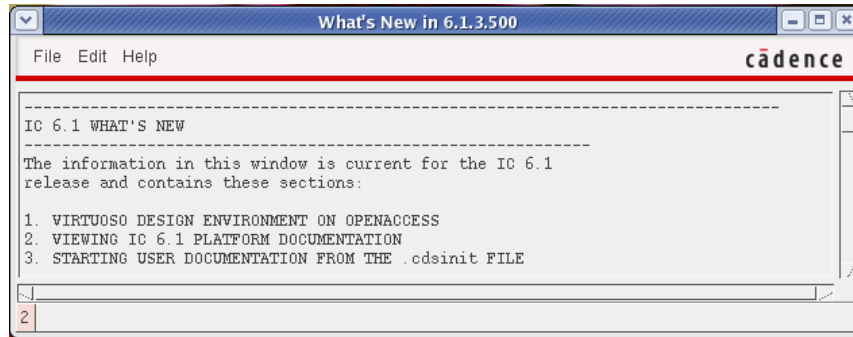3. If the “What’s New ...” window appears, close it with the **File— Close** command.



4. Keep opened CIW window for the labs.
5. The constraint file discussed in Part A can be considered for Analog Design flow.


Lab 1: AN INVERTER

AIM : To simulate the schematic of the CMOS inverter, and then to perform the physical verification for the layout of the same.

TOOL REQUIRED : Cadence Tool

THEORY: The inverter is universally accepted as the most basic logic gate doing a Boolean operation on a single input variable. Fig.1 depicts the symbol, truth table and a general structure of a CMOS inverter. As shown, the simple structure consists of a combination of an pMOS transistor at the top and a nMOS transistor at the bottom.

Schematic Capture

 

Schematic Entry

Creating a New library

1. In the Library Manager, execute **File - New – Library**. The new library form appears.
2. In the “New Library” form, type “**myDesignLib**” in the Name section.




3. In the field of Directory section, verify that the path to the library is set to **~/Database/cadence_analog_labs_613** and click **OK**.

4. In the next “**Technology File for New library**” form, select option **Attach to an existing techfile** and click **OK**.



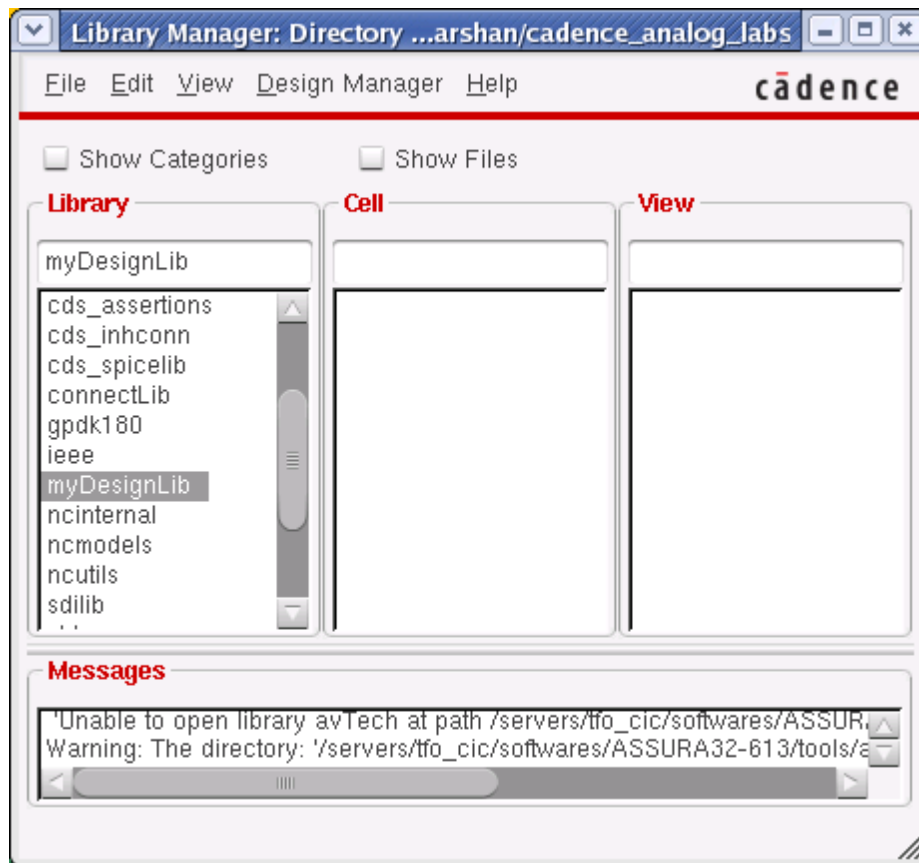
5. In the “**Attach Design Library to Technology File**” form, select **gpd180** from the cyclic field and click **OK**.
6. After creating a new library you can verify it from the library manager.
7. If you right click on the “**myDesignLib**” and select properties, you will find that **gpd180** library is attached as techlib to “**myDesignLib**”.



Creating a Schematic Cellview

In this section we will learn how to open new schematic window in the new “**myDesignLib**” library and build the inverter schematic as shown in the figure at the start of this lab.

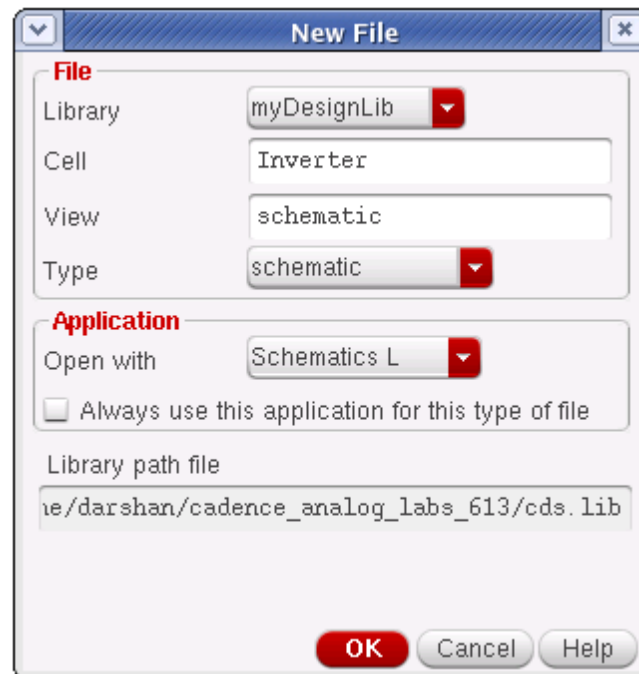1. In the CIW or Library manager, execute **File – New – Cellview**.
2. Set up the New file form as follows:



3. Click **OK** when done the above settings. A blank schematic window for the **Inverter** design appears.

Adding Components to schematic



1. In the Inverter schematic window, click the **Instance** fixed menu icon to display the Add Instance form.
Tip: You can also execute **Create — Instance** or press **i**.

2. Click on the **Browse** button. This opens up a Library browser from which you can select components and the **symbol** view .

3. After completing the Add Instance form, move cursor to the schematic window and click **left** to place a component.

This is a table of components for building the Inverter schematic.

Library name	Cell Name	Properties/Comments
gpd180	pmos	For M0: Model name = pmos1, W= wp, L=180n
gpd180	nmos	For M1: Model name = nmos1, W= 2u, L=180n

4. After entering components, click **Cancel** in the Add Instance form or press **Esc** with your cursor in the schematic window.

Adding pins to Schematic

1. Click the **Pin** fixed menu icon in the schematic window. 

You can also execute **Create — Pin** or press **p**.
The Add pin form appears.

2. Type the following in the Add pin form in the exact order leaving space between the pin names.

Pin Names	Direction
vin	Input
vout	Output

3. Select **Cancel** from the Add – pin form after placing the pins.

Adding Wires to a Schematic

Add wires to connect components and pins in the design.

1. Click the **Wire (narrow)** icon in the schematic window.



You can also press the **w** key, or execute **Create — Wire (narrow)**.

2. In the schematic window, click on a pin of one of your components as the first point for your wiring. A diamond shape appears over the starting point of this wire.
3. Follow the prompts at the bottom of the design window and click **left** on the destination point for your wire. A wire is routed between the source and destination points.
4. Complete the wiring as shown in figure and when done wiring press **ESC** key in the schematic window to cancel wiring

Saving the Design


1. Click the **Check and Save** icon in the schematic editor window.



2. Observe the CIW output area for any errors.

Symbol Creation

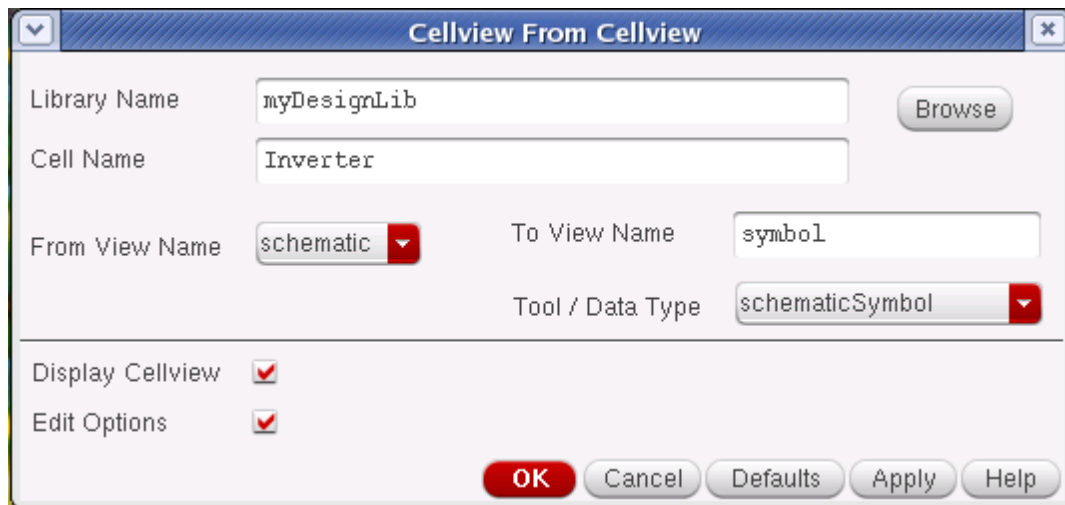
1. In the Inverter schematic window, execute **Create — Cellview — From Cellview**. The **CellviewFromCellview** form appears. With the Edit Options function active, you can control the appearance of the symbol to generate.
2. Verify that the **From View Name** field is set to **schematic**, and the **To View Name** field is set to **symbol**, with the **Tool/Data Type** set as **SchematicSymbol**.



The 'Cellview From Cellview' dialog box is shown. It has a title bar with a dropdown arrow and a close button. The fields are: Library Name (myDesignLib), Cell Name (Inverter), From View Name (schematic), To View Name (symbol), and Tool / Data Type (schematicSymbol). There are checkboxes for 'Display Cellview' and 'Edit Options', both of which are checked. At the bottom are buttons for OK, Cancel, Defaults, Apply, and Help.

3. Click **OK** in the **CellviewFromCellview** form.
The Symbol Generation Form appears.

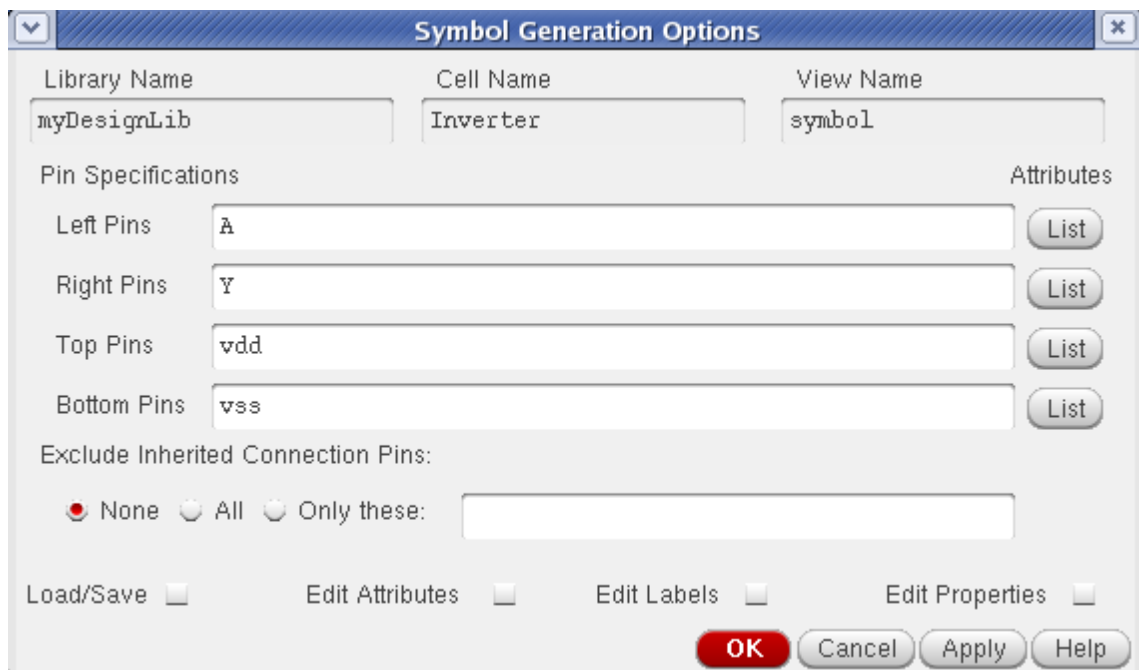
4. Modify the **Pin Specifications** as follows:



The 'Symbol Generation Options' dialog box is shown. It has a title bar with a dropdown arrow and a close button. The fields are: Library Name (myDesignLib), Cell Name (Inverter), and View Name (symbol). Below these are 'Pin Specifications' and 'Attributes'. The 'Pin Specifications' section has four rows: Left Pins (A), Right Pins (Y), Top Pins (vdd), and Bottom Pins (vss). Each row has a 'List' button. Below this is the 'Exclude Inherited Connection Pins' section with three radio buttons: None (selected), All, and Only these: (with an empty text field). At the bottom are checkboxes for Load/Save, Edit Attributes, Edit Labels, and Edit Properties, all of which are unchecked. At the bottom right are buttons for OK, Cancel, Apply, and Help.

5. Click **OK** in the Symbol Generation Options form.

 6. A new window displays an automatically created Inverter symbol as shown here.




Editing a Symbol

In this section we will modify the inverter symbol to look like a Inverter gate symbol.



 
1. Move the cursor over the automatically generated symbol, until the green rectangle is highlighted, click **left** to select it.
2. Click **Delete** icon in the symbol window, similarly select the red rectangle and delete that.
3. Execute **Create – Shape – polygon**, and draw a shape similar to triangle.
4. After creating the triangle press **ESC** key.
5. Execute **Create – Shape – Circle** to make a circle at the end of triangle.
6. You can move the pin names according to the location.
7. Execute **Create — Selection Box**. In the Add Selection Box form, click **Automatic**. A new red selection box is automatically added.
8. After creating symbol, click on the **save** icon in the symbol editor window to save the symbol. In the symbol editor, execute **File — Close** to close the symbol view window.



Building the Inverter_Test Design

Creating the Inverter_TestCellview

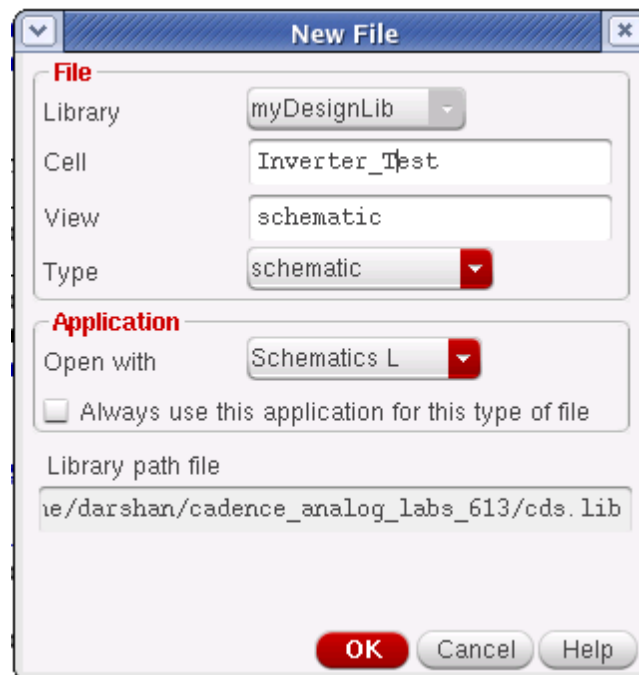1. In the CIW or Library Manager, execute **File—New—Cellview**.
2. Set up the New File form as follows:




3. Click **OK** when done. A blank schematic window for the **Inverter_Test** design appears.

Building the Inverter_TestCircuit

1. Using the component list and Properties/Comments in this table, build the **Inverter_Test** schematic.

Library name	Cellview name	Properties/Comments
myDesignLib	Inverter	Symbol
analogLib	vpulse	v1=0, v2=1.8,td=0 tr=tf=1ns, ton=10n, T=20n
analogLib	vdc, gnd	vdc=1.8

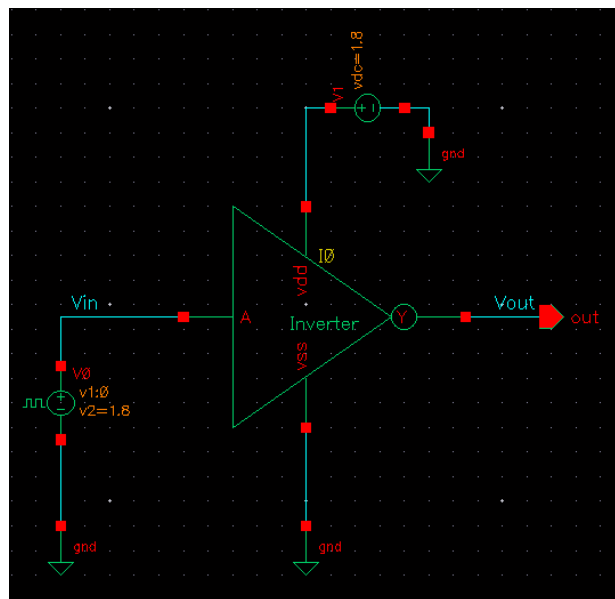2. Add the above components using **Create — Instance** or by pressing **I**.
3. Click the **Wire (narrow)** icon and wire your schematic
4. Click **Create — Wire Name** or press **L** to name the input (**Vin**) and output (**Vout**) wires as in the below schematic.
5. Click on the **Check and Save** icon to save the design
6. The schematic should look like this.



7. Leave your **Inverter_Test** schematic window open for the next section.

Analog Simulation with Spectre

Starting the Simulation Environment

Start the Simulation Environment to run a simulation.

1. In the **Inverter_Test** schematic window, execute

Launch – ADE L

The **Virtuoso Analog Design Environment (ADE)** simulation window appears.

Choosing a Simulator

Set the environment to use the **Spectre® tool**, a high speed, highly accurate analog simulator. Use this simulator with the **Inverter_Test** design, which is made-up of analog components.

1. In the simulation window (ADE), execute

Setup— Simulator/Directory/Host.

2. In the Choosing Simulator form, set the Simulator field to **spectre** (Not spectreS) and click **OK**.

Setting the Model Libraries


The Model Library file contains the model files that describe the nmos and pmos devices during simulation.

1. In the simulation window (ADE),

Execute **Setup - Model Libraries**.

The Model Library Setup form appears. Click the **browse** button to add **gpdn.scs** if not added by default as shown in the **Model Library Setup** form.

 Remember to select the section type as **stat** in front of the gpdn.scsfile. Your Model Library Setup window should now look like the below figure.



To view the model file, highlight the expression in the Model Library File field and

Click **Edit File**.



2. To complete the Model Library Setup, move the cursor and click **OK**.

The Model Library Setup allows you to include multiple model files. It also allows you to use the Edit button to view the model file.

Choosing Analyses

This section demonstrates how to view and select the different types of analyses to complete the circuit when running the simulation.



1. In the Simulation window (ADE), click the **Choose - Analyses** icon. You can also execute **Analyses - Choose**.


The Choosing Analysis form appears. This is a dynamic form, the bottom of the form changes based on the selection above.

2. To setup for transient analysis

a. In the Analysis section select **tran**

b. Set the stop time as **200n**

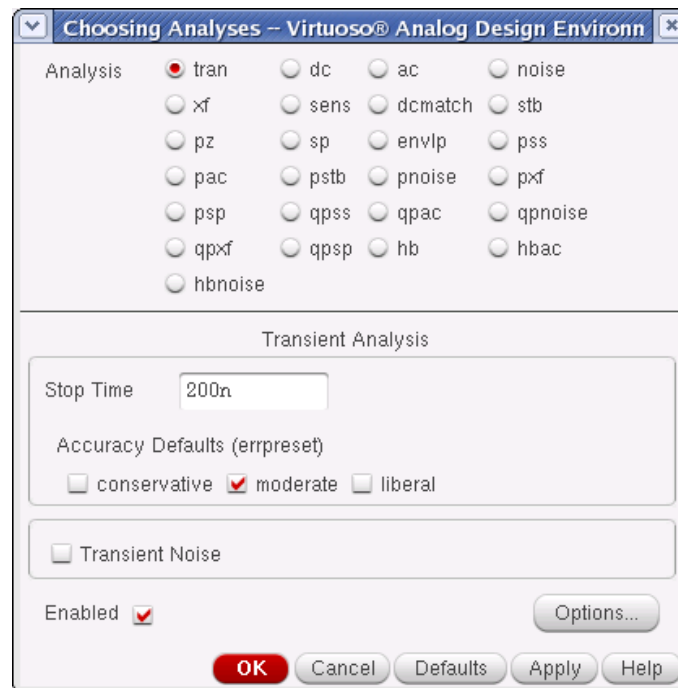c. Click at the **moderate** or **Enabled** button at the bottom, and then click **Apply**.



3. To set up for DC Analyses:

a. In the Analyses section, select **dc**.


b. In the DC Analyses section, turn on **Save DC Operating Point**.

c. Turn on the **Component Parameter**.

d. Double click the **Select Component**, Which takes you to the schematic window.

e. Select input signal **vpulse source** in the test schematic window.

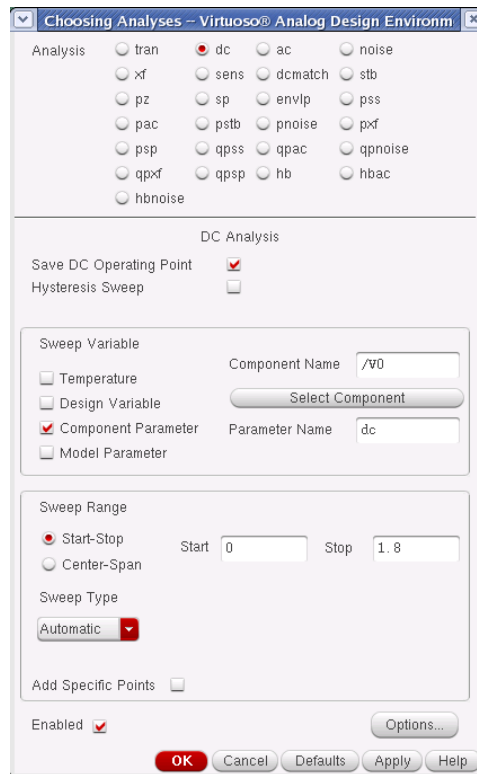- f. Select “**DC Voltage**” in the **Select Component Parameter** form and click OK.
- f. In the analysis form type **start** and **stop** voltages as **0** to **1.8** respectively.
- g. Check the enable button and then click **Apply**.



4. Click **OK** in the Choosing Analyses Form.

Setting Design Variables

Set the values of any design variables in the circuit before simulating. Otherwise, the simulation will not run.



1. In the Simulation window, click the **Edit Variables** icon. The Editing Design Variables form appears.
2. Click **Copy From** at the bottom of the form. The design is scanned and all variables found in the design are listed. In a few moments, the **wpvariable** appears in the Table of Design variables section.
3. Set the value of the **wpvariable**:
With the **wpvariable** highlighted in the Table of Design Variables,


Value(Expr)	2u
-------------	----

Click **Change** and notice the update in the Table of Design Variables.


4. Click **OK** or **Cancel** in the Editing Design Variables window.


Selecting Outputs for Plotting

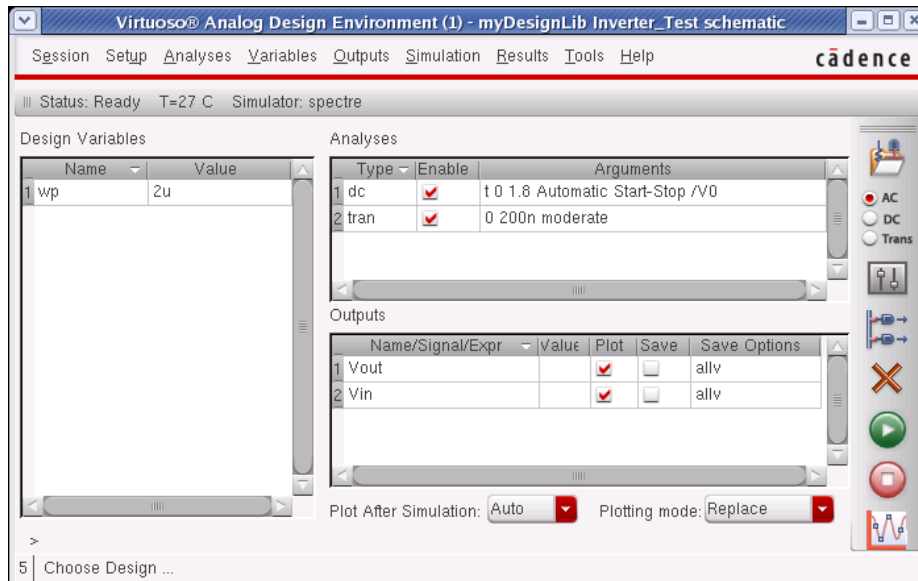1. Execute **Outputs – To be plotted – Select on Schematic** in the simulation window.
2. Follow the prompt at the bottom of the schematic window, Click on output net **Vout**, input net **Vin** of the Inverter. Press **ESC** with the cursor in the schematic after selecting it.



Running the Simulation

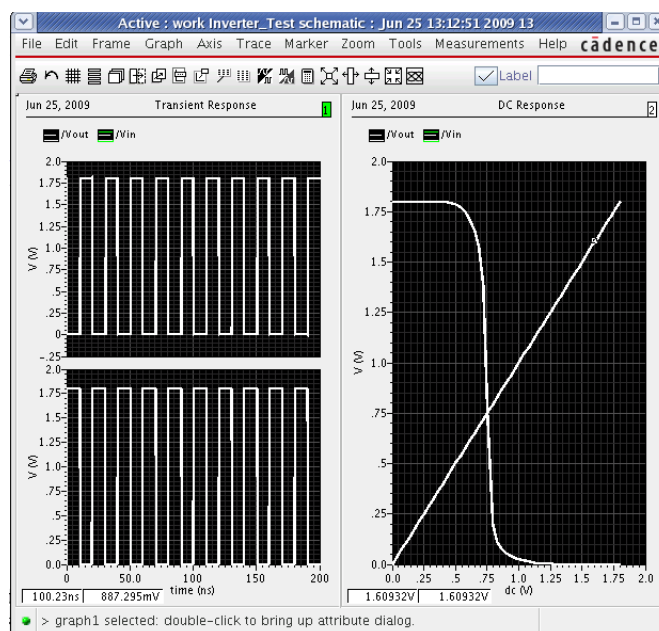1. Execute **Simulation – Netlist and Run** in the simulation window to start the  Simulation or the icon, this will create the netlist as well as run the simulation.
2. When simulation finishes, the Transient, DC plots automatically will be popped up along with log file.



Saving the Simulator State

We can save the simulator state, which stores information such as model library file, outputs, analysis, variable etc. This information restores the simulation environment without having to type in all of setting again.

1. In the Simulation window, execute **Session – Save State**. The Saving State form appears.
2. Set the **Save as** field to **state1_inv** and make sure all options are selected under what to save field.
3. Click **OK** in the saving state form. The Simulator state is saved.

Loading the Simulator State

1. From the ADE window execute **Session – Load State**. In the Loading State window, set the State name to **state1_inv** as shown



2. Click **OK** in the Loading State window.

Parametric Analysis

Parametric Analysis yields information similar to that provided by the Spectre® sweep feature, except the data is for a full range of sweeps for each parametric step. The Spectre sweep feature provides sweep data at only one specified condition.

You will run a parametric DC analysis on the **wp** variable, of the PMOS device of the Inverter design by sweeping the value of **wp**.

Run a simulation before starting the parametric tool. You will start by loading the state from the previous simulation run.

Run the simulation and check for errors. When the simulation ends, a single waveform in the waveform window displays the DC Response at the **Vout** node.

Starting the Parametric Analysis Tool

1. In the Simulation window, execute **Tools—Parametric Analysis**. The Parametric Analysis form appears.

2. In the Parametric Analysis form, execute **Setup—Pick Name For Variable—Sweep 1**.

A selection window appears with a list of all variables in the design that you can sweep. This list includes the variables that appear in the Design Variables section of the Simulation window.


3. In the selection window, double click left on **wp**. The Variable Name field for Sweep 1 in the Parametric Analysis form is set to **wp**.

4. Change the Range Type and Step Control fields in the Parametric Analysis form as shown below:

Range Type **From/To** From **1u** To **10u**


Step Control **Auto** Total Steps **10**

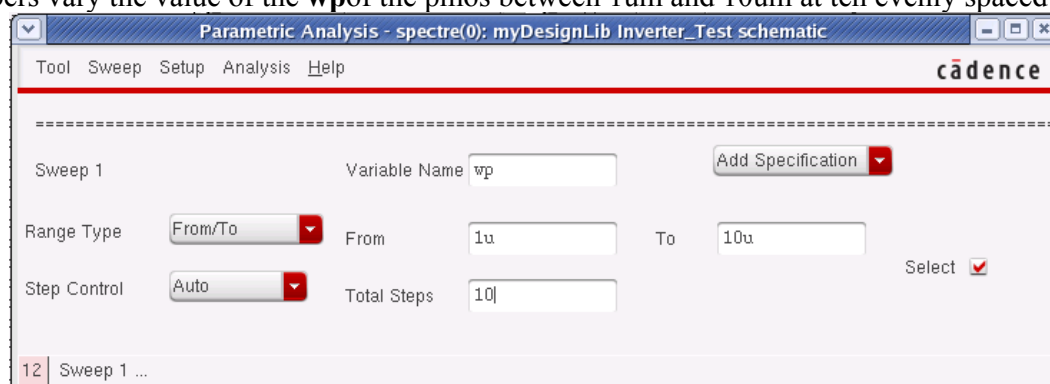These numbers vary the value of the **wp** of the pmos between 1um and 10um at ten evenly spaced intervals.



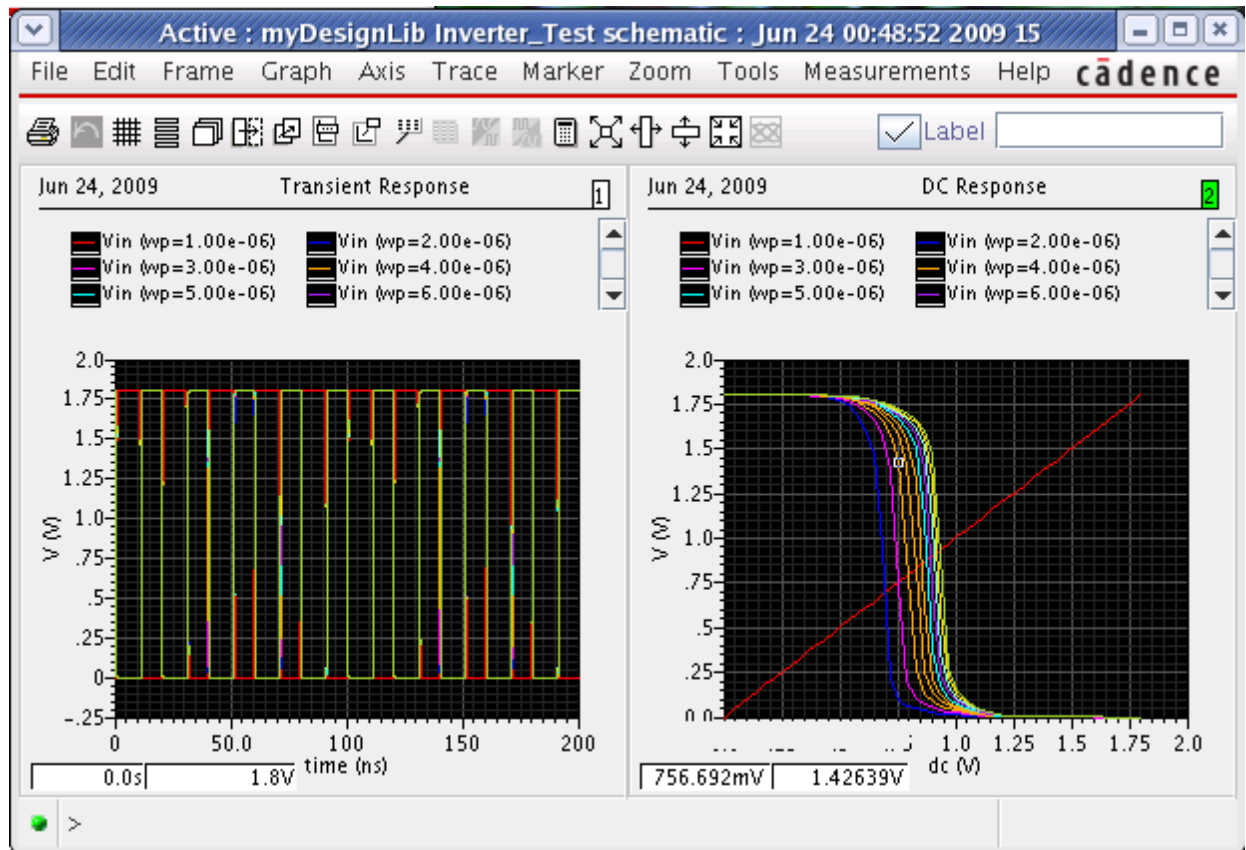5. Execute Analysis—Start.


The Parametric Analysis window displays the number of runs remaining in the analysis and the current value of the swept variable(s). Look in the upper right corner of the window. Once the runs are completed the waves can window comes up with the plots for different runs.



Creating Layout View of Inverter

1. From the **Inverter** schematic window menu execute **Launch – Layout XL**. A **Startup Option** form appears.
 2. Select **Create New** option. This gives a New Cell View Form
 3. Check the Cellname(**Inverter**), Viewname(**layout**).
 4. Click **OK** from the New Cellview form.
- LSW and a blank layout window appear along with schematic window

Adding Components to Layout

1. Execute **Connectivity – Generate – All from Source** or click the icon  in the layout editor window, **Generate Layout** form appears. Click **OK** which imports the schematic components in to the Layout window automatically.
2. Re arrange the components with in PR-Boundary as shown in the next page.
3. To rotate a component, Select the component and execute **Edit –Properties**. Now select the degree of rotation from the property edit form.




4. To Move a component, Select the component and execute **Edit -Move** command.

Making interconnection

1. Execute **Connectivity –Nets – Show/Hide selected Incomplete Nets** or click the icon in the Layout Menu.
2. Move the mouse pointer over the device and click **LMB** to get the connectivity information, which shows the guide lines (or flight lines) for the inter connections of the components.
3. From the layout window execute **Create – Shape – Path/ Create wire** or **Create – Shape – Rectangle** (for vdd and gnd bar) and select the appropriate Layers from the **LSW** window and Vias for making the inter connections

Creating Contacts/Vias


You will use the contacts or vias to make connections between two different layers.

1. Execute **Create-Via** or select  command to place different Contacts, as given in below table

Connection	Contact Type
For Metal1- Poly Connection	Metal1-Poly
For Metal1- Psubstrate Connection	Metal1-Psub
For Metal1- Nwell Connection	Metal1-Nwell

Saving the design

 1. Save your design by selecting **File — Save** or click  to save the layout, and layout should appear as below.



Physical Verification

Assura DRC


Running a DRC

1. Open the Inverter layout from the CIW or library manager if you have closed that. Press **shift – f** in the layout window to display all the levels.

2. Select **Assura - Run DRC** from layout window.

The DRC form appears. The Library and Cellname are taken from the current design window, but rule file may be missing. Select the Technology as **gpd180**. This automatically loads the rule file.

Your DRC form should appear like this

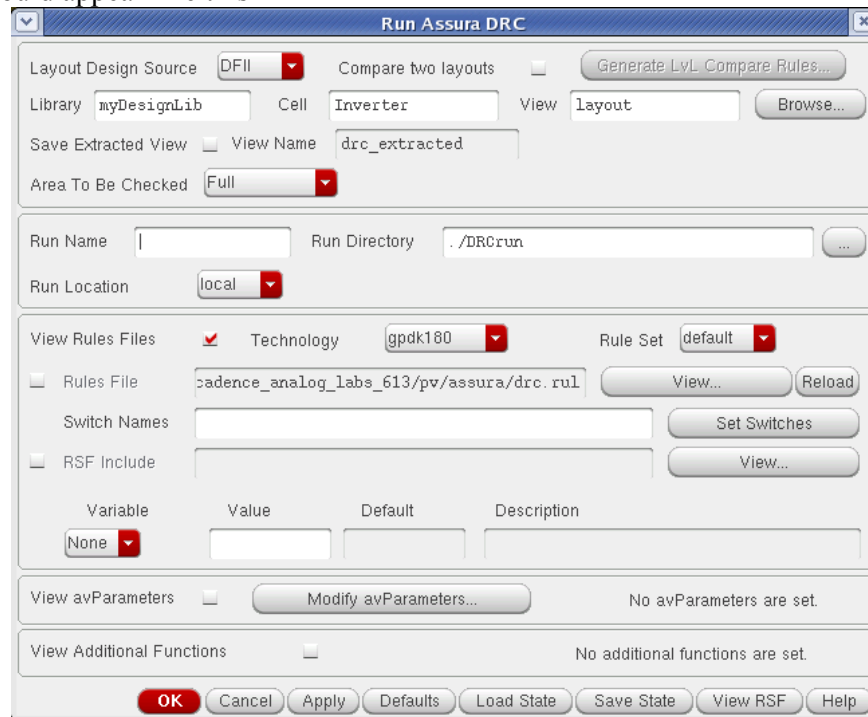

Setting up the Technology libraries(if not present)

Choose **Assura** from layout window-**Technology**, set path to **gpd180**.

3. Click **OK** to start DRC.

4. A Progress form will appear. You can click on the watch log file to see the log file.

5. When DRC finishes, a dialog box appears asking you if you want to view your DRC results, and then click **Yes** to view the results of this run.

6. If there any DRC error exists in the design **View Layer Window (VLW)** and **Error Layer Window (ELW)** appears. Also the errors highlight in the design itself.

7. Click **View – Summary** in the ELW to find the details of errors.

8. You can refer to rule file also for more information, correct all the DRC errors and **Re – run** the DRC.

9. If there are no errors in the layout then a dialog box appears with **No DRC errors found** written in it, click on **close** to terminate the DRC run.

ASSURA LVS

In this section we will perform the LVS check that will compare the schematic netlist and the layout netlist.

Running LVS

1. Select **Assura – Run LVS** from the layout window.

The Assura Run LVS form appears. It will automatically load both the schematic and layout view of the cell.

2. Change the following in the form and click **OK**

3. The LVS begins and a Progress form appears.

4. If the schematic and layout matches completely, you will get the form displaying **Schematic and Layout Match**.

5. If the schematic and layout do not match, a form informs that the LVS completed successfully and asks if you want to see the results of this run.

6. Click **Yes** in the form.

LVS debug form appears, and you are directed into LVS debug environment.

7. In the **LVS debug form** you can find the details of mismatches and you need to correct all those mismatches and **Re – run** the LVS till you will be able to match the schematic with layout.

Run Assura LVS

Schematic Design Source: **DFII** Use Existing Netlist ☐ Netlisting Options...

Library: **myDesignLib** Cell: **Inverter** View: **schematic** Browse...

Layout Design Source: **DFII** Use Existing Extracted Netlist ☐

Library: **myDesignLib** Cell: **Inverter** View: **layout** Browse...

Run Name: Run Directory: **./LVS** ...

Run Location: **local**

View Rules Files: ☒ Technology: **gpd180** Rule Set: **default**

Extract Rules: ☐ **ance_analog_labs_613/pv/assura/extract.rul** View... Reload

Compare Rules: ☐ **an/cadence_analog_labs_613/pv/assura/compare.rul** View...

Switch Names: Set Switches

Binding File(s): View...

RSF Include: View...

Variable	Value	Default	Description
None	<input type="text"/>	<input type="text"/>	<input type="text"/>

View avParameters: ☐ Modify avParameters... 7 avParameters are set.

View avCompareRules: ☐ Modify avCompareRules... 1 avCompare rule is set.

View Additional Functions: ☐ No additional functions are set.

OK Cancel Apply Defaults Load State Save State View RSF Help


Assura RCX

In this section we will extract the RC values from the layout and perform analog circuit simulation on the designs extracted with RCX.


Before using RCX to extract parasitic devices for simulation, the layout should match with schematic completely to ensure that all parasites will be backannotated to the correct schematic nets.

Running RCX

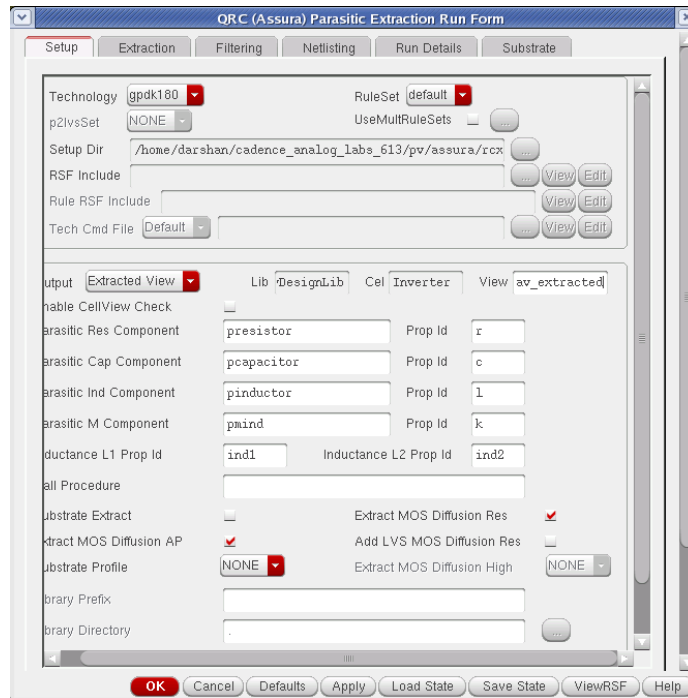1. From the layout window execute **Assura – Run RCX**.
2. Change the following in the Assura parasitic extraction form. Select **output** type under **Setup** tab of the form.




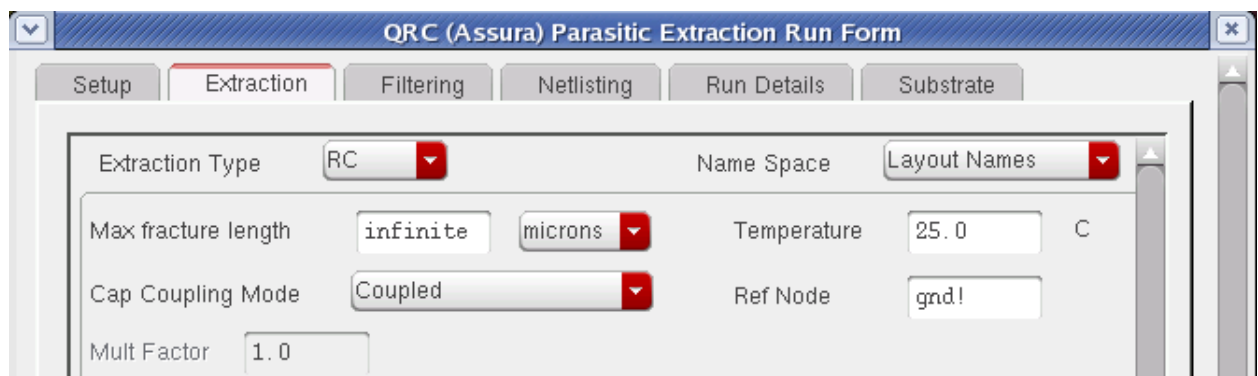3. In the **Extraction** tab of the form, choose Extraction type, Cap Coupling Mode and specify the Reference node for extraction



4. In the **Filtering** tab of the form, **Enter Power Nets** as **vdd!,vss!** and **Enter Ground Nets** as **gnd!**
Click **OK** in the Assura parasitic extraction form when done. The RCX progress form appears, in the progress form click **Watch log file** to see the output log file.

 
5. When RCX completes, a dialog box appears, informs you that **Assura RCX run Completed successfully**.
6. You can open the **av_extracted** view from the library manager and view the parasitic.




Creating the Configuration View

In this section we will create a config view and with this config view we will run the simulation with and without parasitic.

 
1. In the CIW or Library Manager, execute **File – New – Cellview**
2. In the Create New file form, set the following:



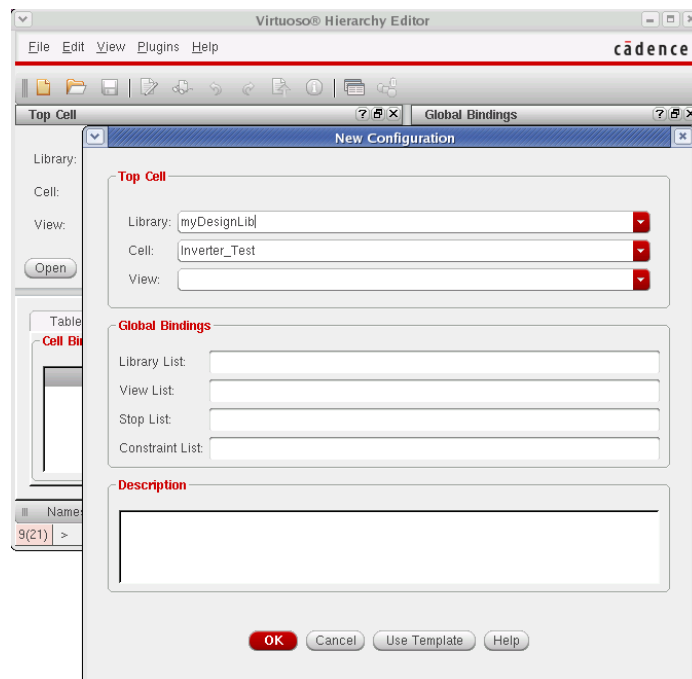
3. Click **OK** in create **New File** form. The **Hierarchy Editor** form opens and a **New Configuration** form opens in front of it.



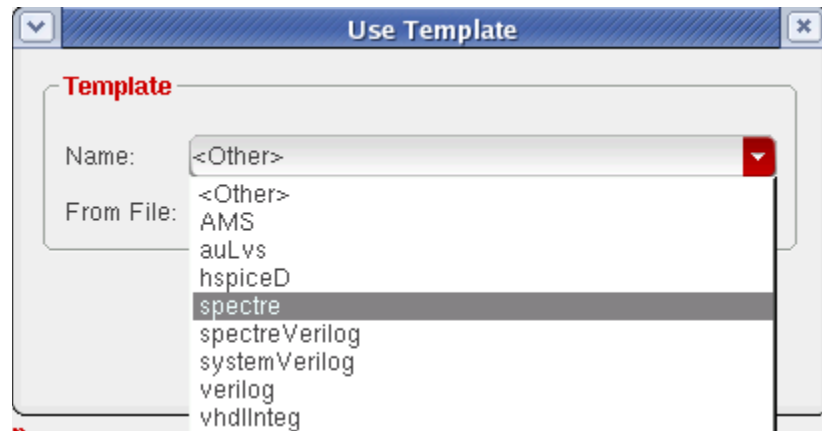
4. Click **Use template** at the bottom of the **New Configuration** form and select **Spectre** in the cyclic field and click **OK**. The Global Bindings lists are loaded from the template.



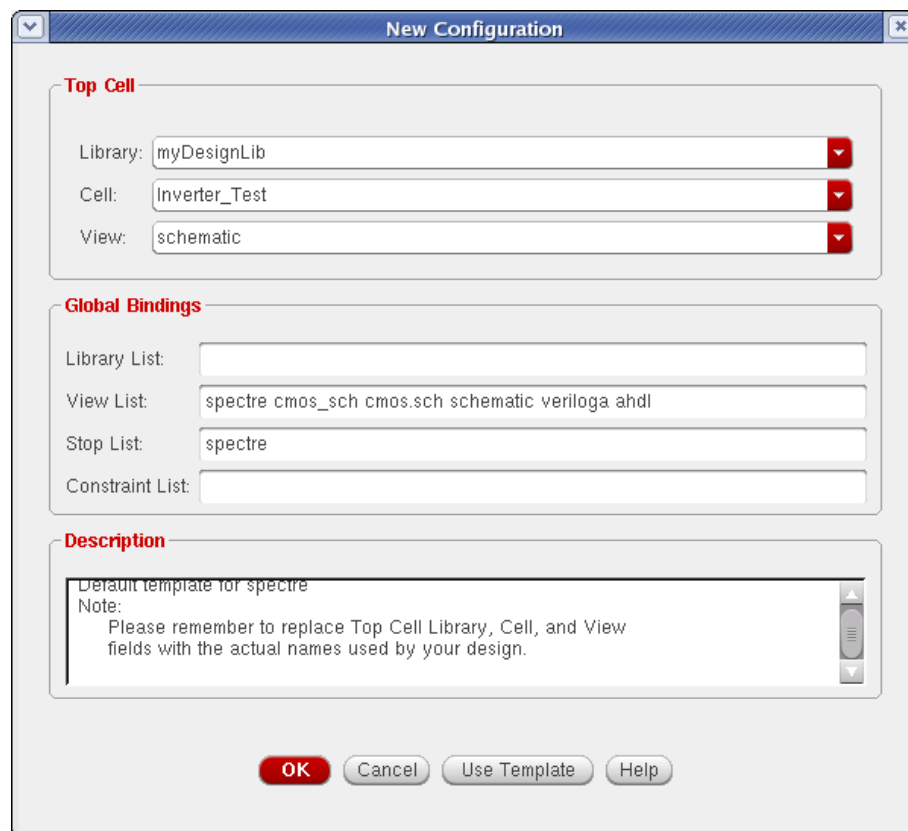
5. Change the **Top Cell View** to **schematic** and remove the default entry from the **Library List** field.
6. Click **OK** in the New Configuration form.



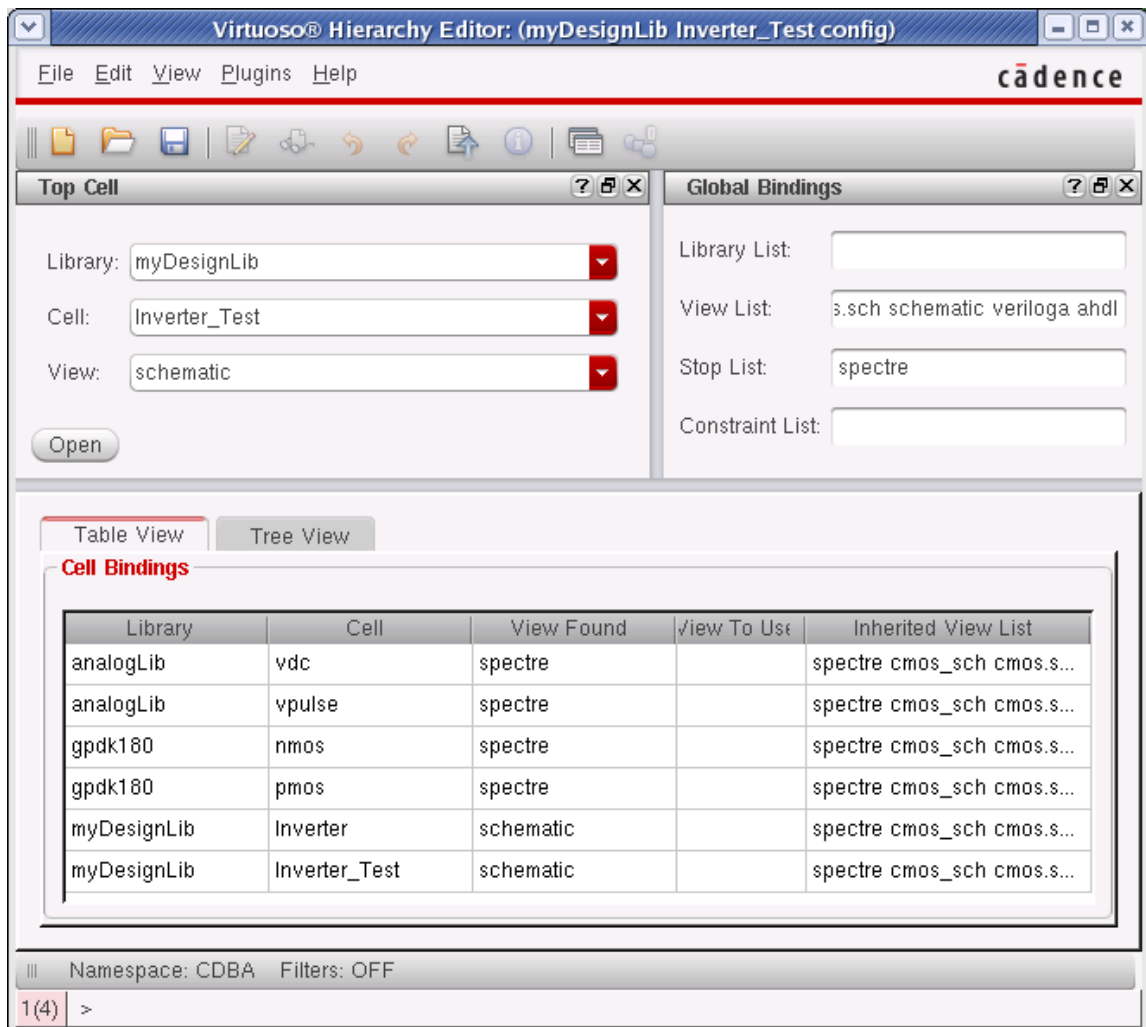7. The hierarchy editor displays the hierarchy for this design using table format.



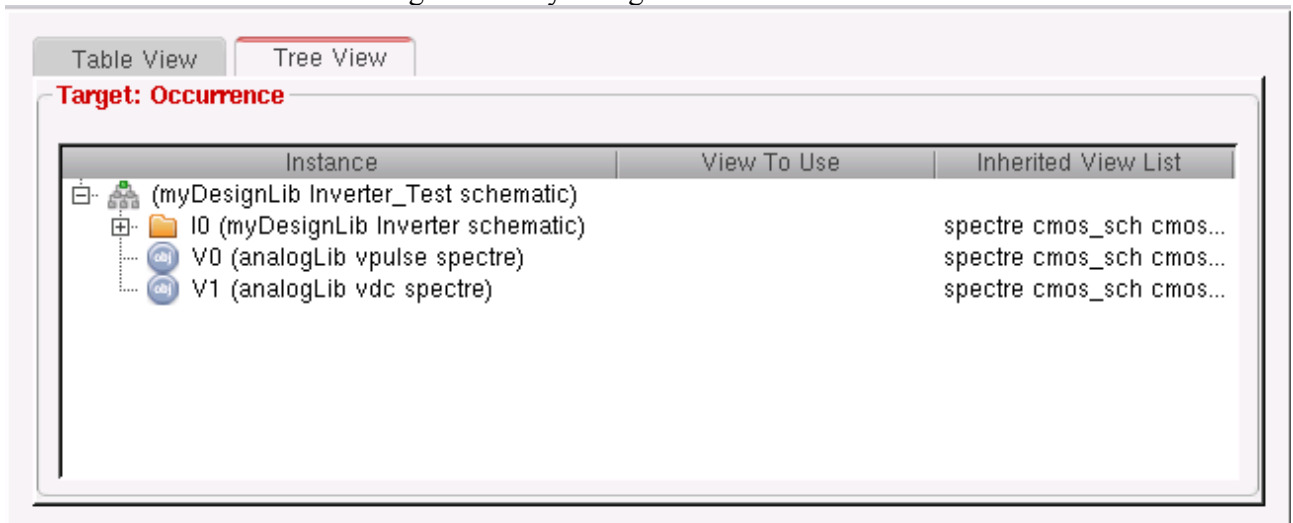8. Click the **Tree View** tab. The design hierarchy changes to tree format. The form should look like this:




Save the current configuration



9. Close the Hierarchy Editor window. Execute **File – Close Window**

To run the Circuit without Parasites

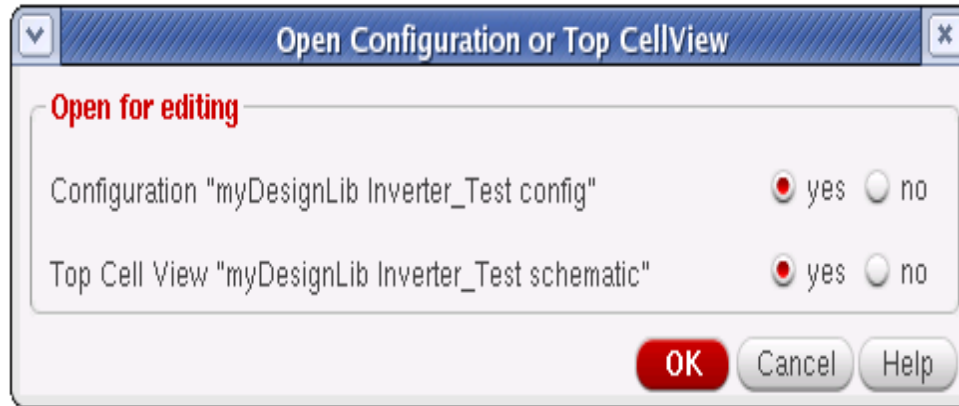1. From the Library Manager open **Inverter_TestConfig** view.
Open Configuration or Top cellview form appear



2. In the form, turn on the both cyclic buttons to **Yes** and click **OK**.

The Inverter_Test schematic and Inverter_Testconfig window appears. Notice the window banner of schematic also states **Config: myDesignLibInverter_Testconfig**.

3. Execute **Launch – ADE L** from the schematic window.


4. Now you need to follow the same procedure for running the simulation. Executing **Session– Load state**, the Analog Design Environment window loads the previous state.




5. Click **Netlist and Run** icon to start the simulation. The simulation takes a few seconds and then waveform window appears.

6. In the CIW, note the netlisting statistics in the **Circuit inventory** section. This list includes all nets, designed devices, source and loads. There are no parasitic components. Also note down the circuit inventory section.

Measuring the Propagation Delay

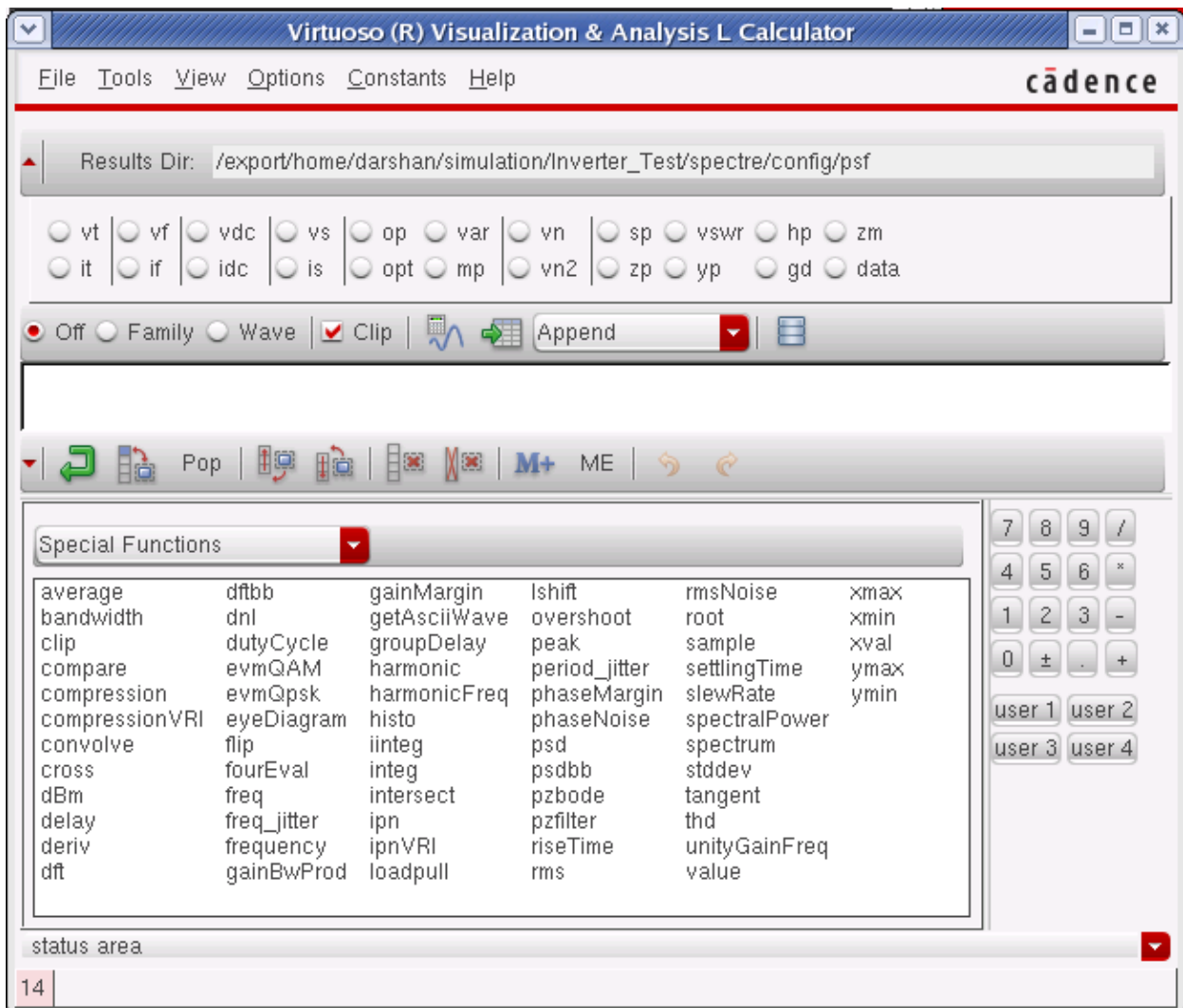1. In the waveform window execute **Tools – Calculator** 
2. The calculator window appears



From the functions select **delay**, this will open the delay data panel.


3. Place the cursor in the text box for Signal1, select the **wave** button and select the input waveform from the waveform window.
4. Repeat the same for Signal2, and select the output waveform.
5. Set the **Threshold value 1** and **Threshold value 2** to 0.9, this directs the calculator to calculate delay at 50% i.e. at 0.9 volts.
6. Execute **OK** and observe the expression created in the calculator buffer.
7. Click on **Evaluate the buffer icon** to perform the calculation, note down the value returned after execution.
8. Close the calculator window

To run the Circuit with Parasites

In this exercise, we will change the configuration to direct simulation of the **av_extracted** view which contains the parasites.

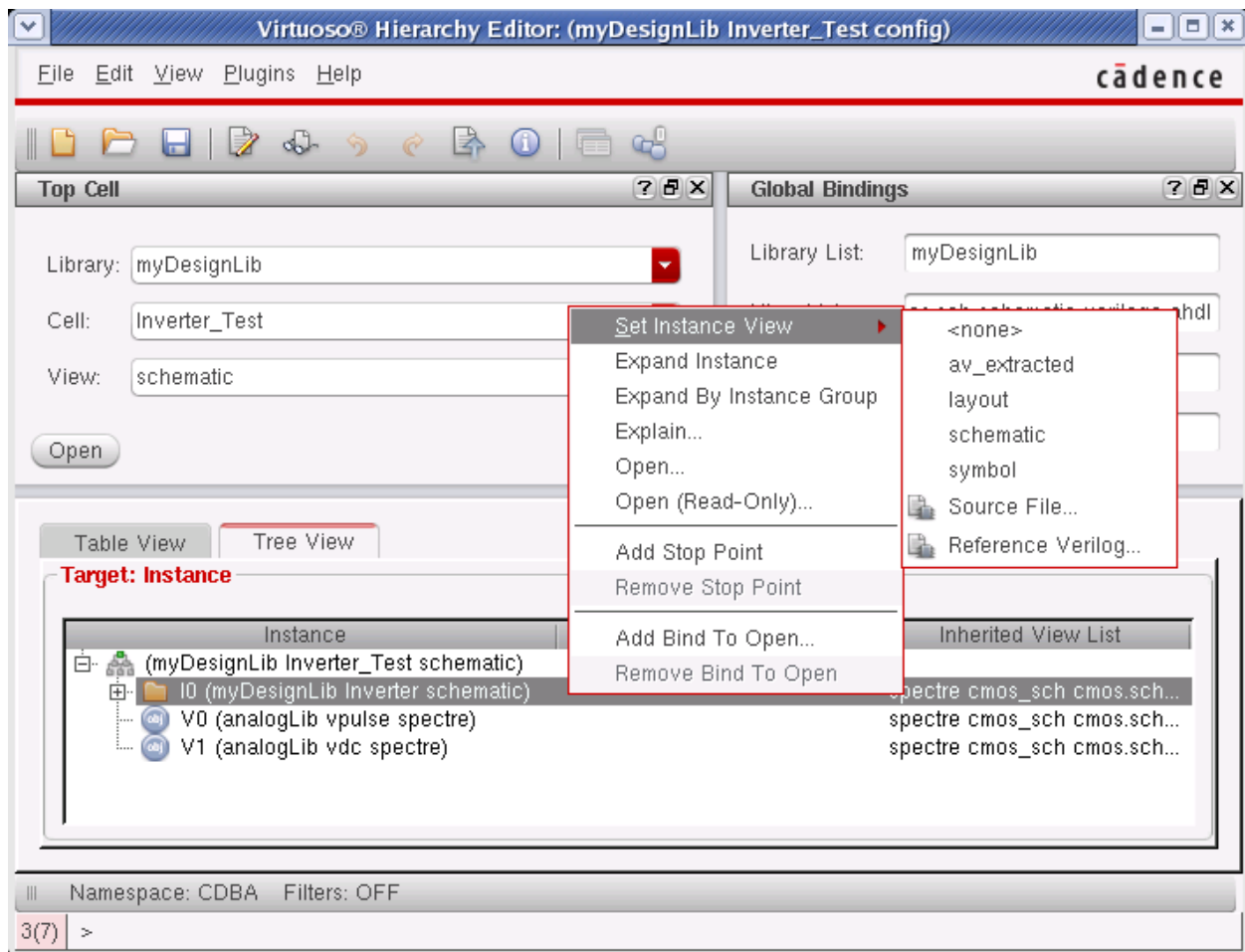1. Open the same Hierarchy Editor form, which is already set for Inverter_Testconfig.
2. Select the **Tree View** icon: this will show the design hierarchy in the tree format.
3. Click **right** mouse on the Inverter schematic.

A pull down menu appears. Select **av_extracted** view from the **Set Instance view** menu, the View to use column now shows av_extracted view



4. Click on the **Recompute the hierarchy** icon,  the configuration is now updated from schematic to av_extracted view.

5. From the **Analog Design Environment** window click **Netlist and Run**  to start the simulation again.


6. When simulation completes, note the **Circuit inventory conditions**, this time the list shows all nets, designed devices, sources and parasitic devices as well.

7. Calculate the delay again and match with the previous one. Now you can conclude how much delay is introduced by these parasites, now our main aim should to minimize the delay due to these parasites so number of iteration takes place for making an optimize layout.

Generate Streaming Data

Streaming Out the Design

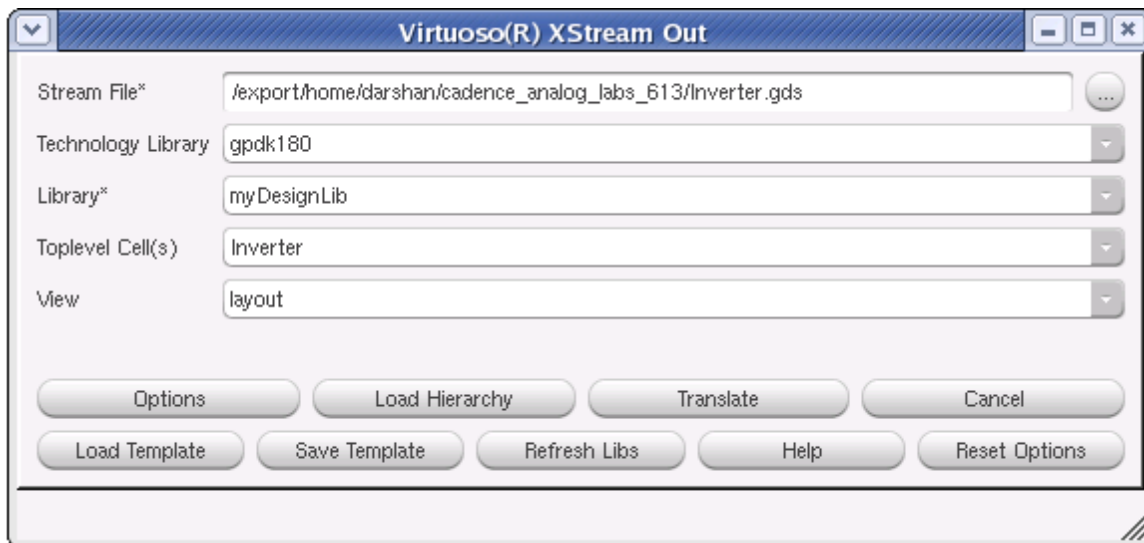
1. Select **File – Export – Stream** from the CIW menu and **Virtuoso Xstream out** form appears change the following in the form.



2. Click on the **Options** button.
3. In the **StreamOut-Options** form select under **Layers** tab and click **OK**.
4. In the **Virtuoso XStream Out** form, click **Translate** button to start the stream translator.
5. The stream file **Inverter.gds** is stored in the specified location.

Streaming In the Design

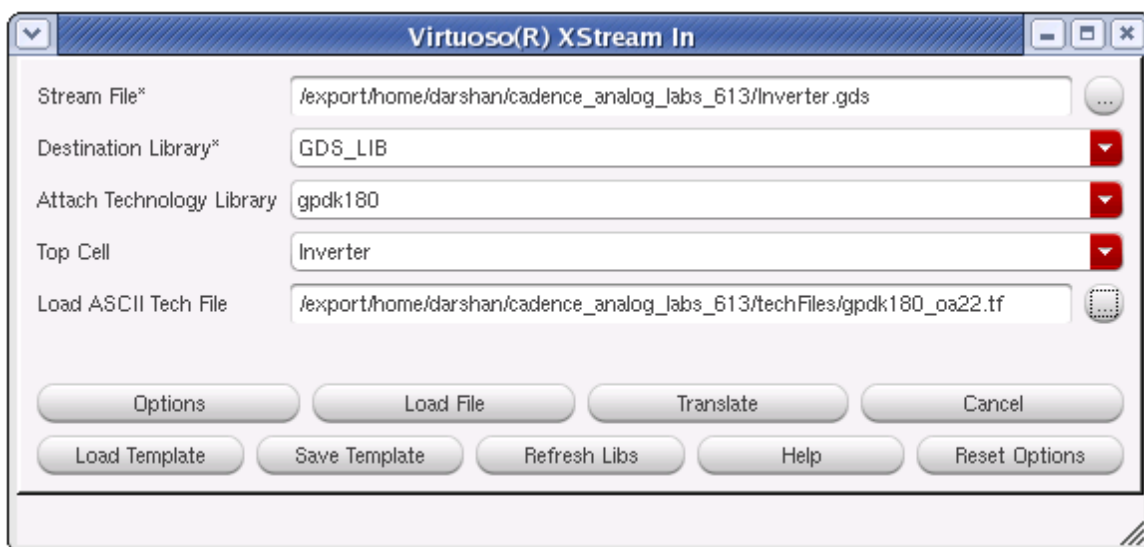1. Select **File – Import – Stream** from the CIW menu and change the following in the form.



You need to specify the **gpdk180_oa22.tf** file. This is the entire technology file that has been dumped from the design library.

2. Click on the **Options** button.
3. In the **StreamOut-Options** form select under **Layers** tab and click **OK**.
4. In the **Virtuoso XStream Out** form, click **Translate** button to start the stream translator.
5. From the Library Manager open the **Inverter** cellview from the **GDS_LIB** library and notice the design.

RESULT:

- a. The schematic for the inverter is drawn and verified the following: DC Analysis, Transient Analysis
- b. The Layout for the inverter is drawn and verified the DRC, LVS, RC Extraction


Lab 2a: COMMON SOURCE AMPLIFIER

AIM: To simulate the schematic of the Common Source Amplifier, and then to perform the physical verification for the layout of the same.

TOOL REQUIRED: Cadence Tool

THEORY: In electronics, a common-source amplifier is one of three basic single-stage field-effect transistor (FET) amplifier topologies, typically used as a voltage or transconductance amplifier. The easiest way to tell if a FET is common source, common drain, or common gate is to examine where the signal enters and leaves. The remaining terminal is what is known as "common". In this example, the signal enters the gate, and exits the drain. The only terminal remaining is the source. This is a common-source FET circuit. The analogous bipolar junction transistor circuit is the common-emitter amplifier. The common-source (CS) amplifier may be viewed as a transconductance amplifier or as a voltage amplifier. (See classification of amplifiers). As a transconductance amplifier, the input voltage is seen as modulating the current going to the load. As a voltage amplifier, input voltage modulates the amount of current flowing through the FET, changing the voltage across the output resistance according to Ohm's law. However, the FET device's output resistance typically is not high enough for a reasonable transconductance amplifier (ideally infinite), nor low enough for a decent voltage amplifier (ideally zero). Another major drawback is the amplifier's limited high-frequency response.

Schematic Capture

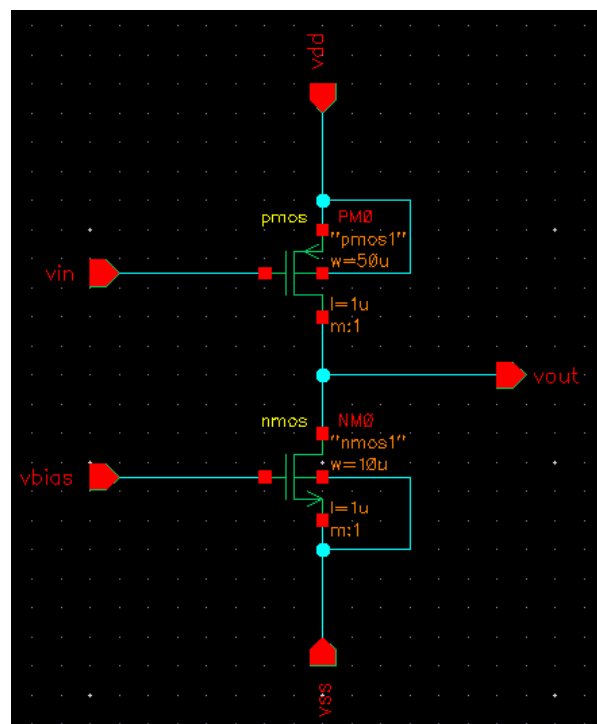

Schematic Entry


This is a table of components for building the Common Source Amplifier schematic

Library name	Cell Name	Properties/Comments
gpd180	pmos	Model Name = pmos1; W= 50u ; L= 1u
gpd180	nmos	Model Name =nmos1; W= 10u ; L= 1u

Type the following in the ADD pin form in the exact order leaving space between the pin names

Pin Names	Direction
vin vbias	Input
vout	Output
vddvss	Input

Symbol Creation

 


Building the Common Source Amplifier Test Design


Using the component list and Properties/Comments in the table, build the cs-amplifier_test schematic as shown below.


Library name	Cell Name	Properties/Comments
myDesignLib	cs_amplifier	Symbol
analogLib	vsin	Define pulse specification as

		AC Magnitude= 1; DC Voltage= 0; Offset Voltage= 0; Amplitude= 5m Frequency= 1K
analogLib	Vdd,vss,gnd	vdd=2.5 ; vss= -2.5

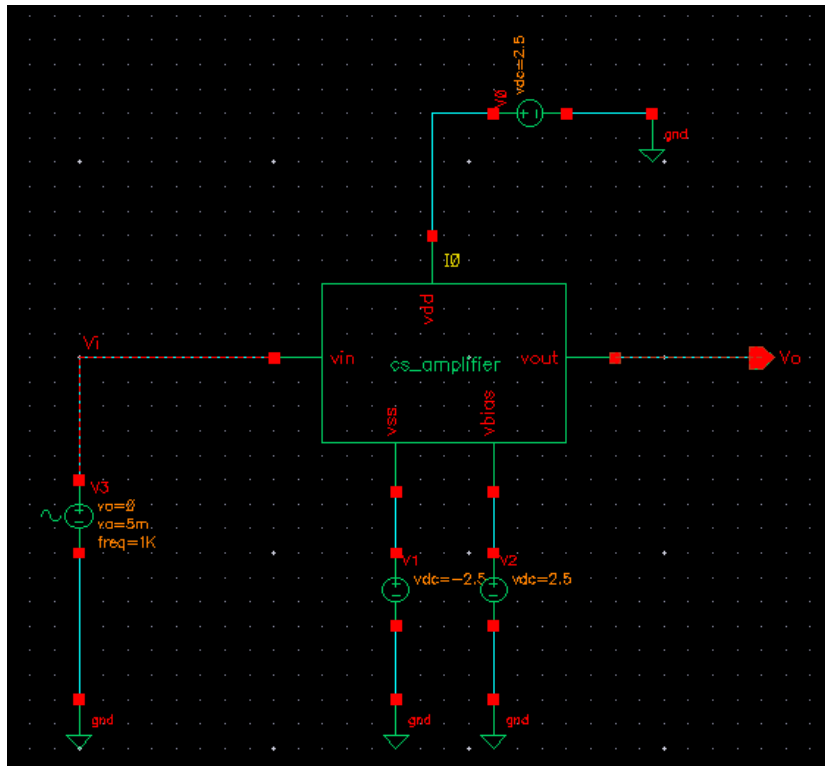

Analog Simulation with Spectre

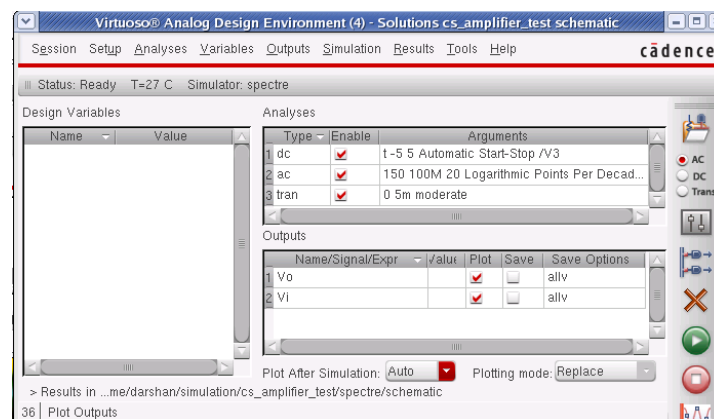


 

Creating a layout view of Common Source Amplifier

Complete the DRC, LVS check using the Assura tool.

 Extract RC parasites for back annotation and Re-simulation



RESULT:

- The schematic for the common source amplifier is drawn and verified the following: DC Analysis, AC Analysis, and Transient Analysis.
- The Layout for the common source amplifier is drawn and verified the DRC, LVS, and RC Extraction.

Lab 2b: Common Drain Amplifier

AIM: To simulate the schematic of the Common Drain Amplifier, and then to perform the physical verification for the layout of the same.


TOOL REQUIRED: Cadence Tool

THEORY: Common drain amplifier is a source follower or buffer amplifier circuit using a MOSFET. The output is simply equal to the input minus about 2.2V. The advantage of this circuit is that the MOSFET can provide current and power gain; the MOSFET draws no current from the input. It provides low output impedance to any circuit using the output of the follower, meaning that the output will not drop under load.

Its output impedance is not as low as that of an emitter follower using a bipolar transistor (as you can verify by connecting a resistor from the output to -15V), but it has the advantage that the input impedance is infinite. The MOSFET is in saturation, so the current across it is determined by the gate-source voltage. Since a current source keeps the current constant, the gate-source voltage is also constant.

Schematic Capture

Circuit diagram in schematic entry

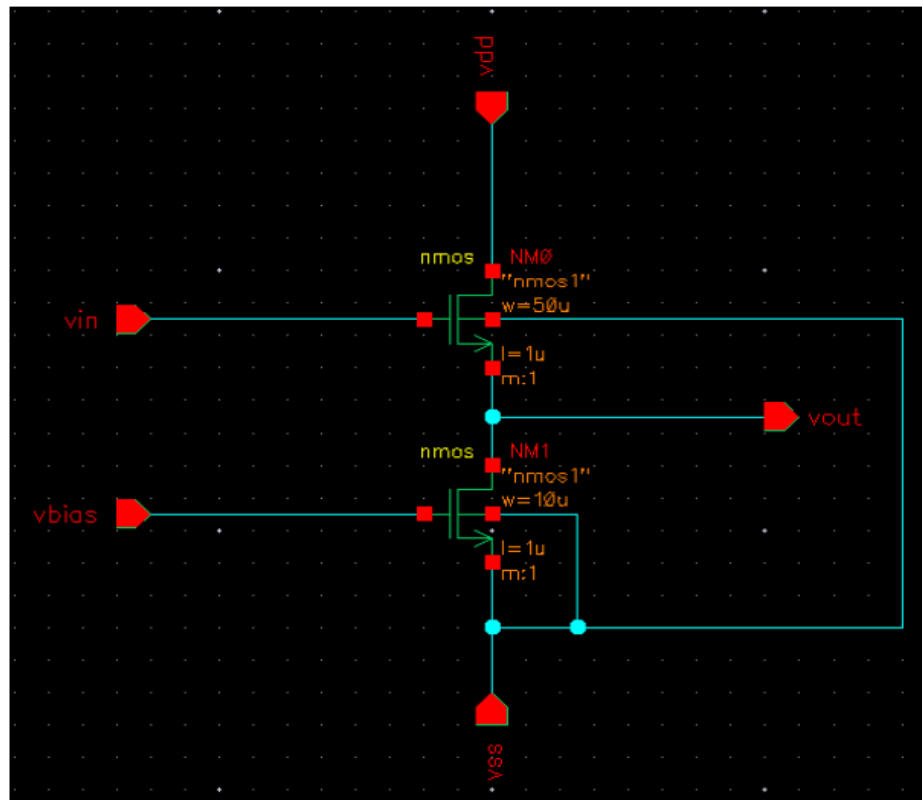


This is a table of components for building the Common Drain Amplifier schematic

Library name	Cell Name	Properties/Comments
gpd180	nmos	Model Name = nmos1; W= 50u ; L= 1u
gpd180	nmos	Model Name = nmos1; W= 10u ; L= 1u

Type the following in the ADD pin form in the exact order leaving space between the pin names.

Pin Names	Direction
vin, vbias	Input
vout	Output
vdd vss	Input

Symbol Creation

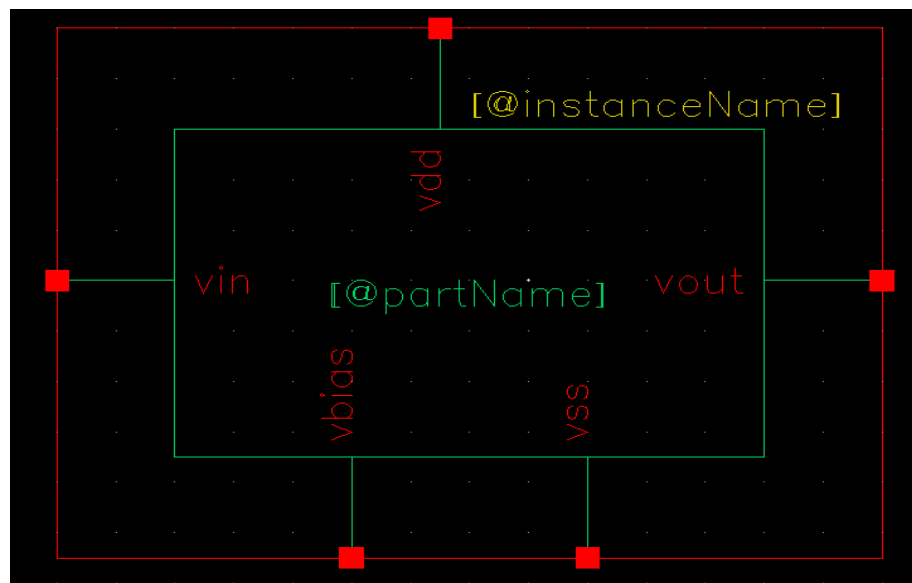


Building Common Drain Amplifier test Design



Using the component list and Properties/Comments in the table, build the cd-amplifier_test schematic as shown below.

Library name	Cellview name	Properties/Comments
myDesignLib	cd_amplifier	Symbol
analogLib	vsin	Define pulse specification as AC Magnitude= 1; DC Voltage= 0; Offset Voltage= 0; Amplitude= 5m; Frequency= 1K
analogLib	vdd,vss,gnd	vdd=2.5 ; vss= -2.5

Test Circuit

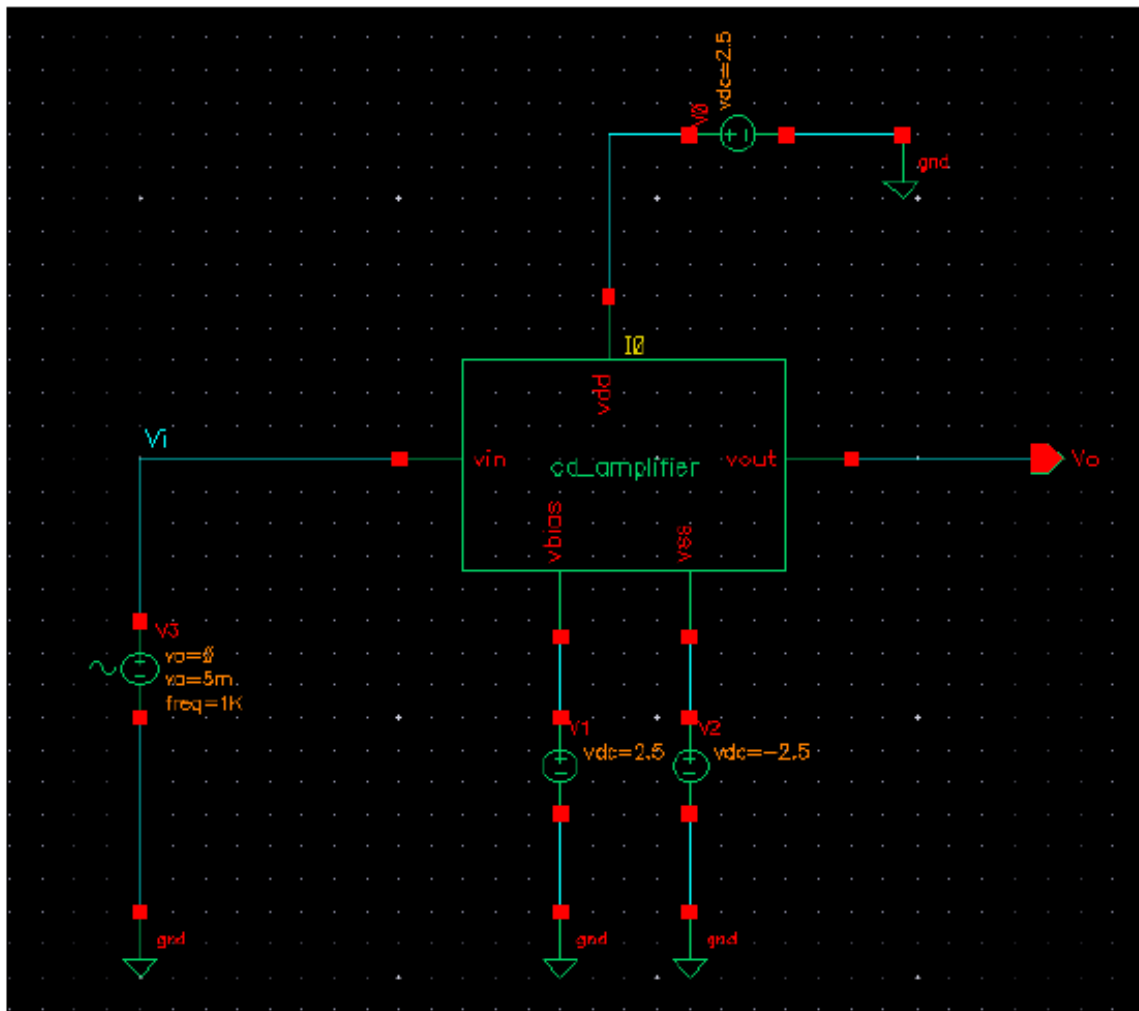


Analog simulation with spectre

 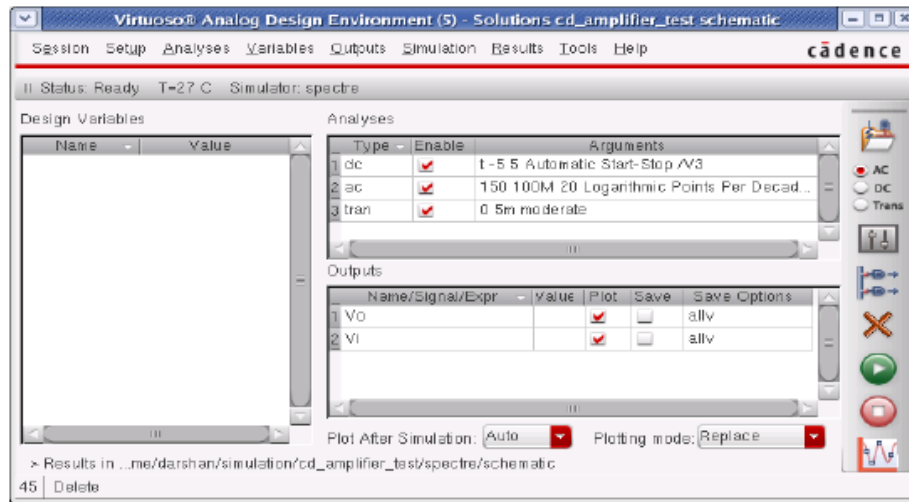

Creating a layout view of Common Drain Amplifier

Complete the DRC, LVS check using the Assura tool.

Extract RC parasites for back annotation and Re-simulation.

 **RESULT:**

- The schematic for the common drain amplifier is drawn and verified the following: DC Analysis, DC Analysis, and Transient Analysis.
- The Layout for the common drain amplifier is drawn and verified the DRC, LVS, and RC Extraction.

AIM : To simulate the schematic of the differential amplifier, and then to perform the physical verification for the layout of the same.

THEORY : The differential amplifier is probably the most widely used circuit building block in analog integrated circuits, principally op amps. We had a brief glimpse at one back in Chapter 3 section 3.4.3 when we were discussing input bias current. The differential amplifier can be implemented with BJTs or MOSFETs. A differential amplifier multiplies the voltage difference between two inputs ($V_{in+} - V_{in-}$) by some constant factor A_d , the differential gain. It may have either one output or a pair of outputs where the signal of interest is the voltage difference between the two outputs. A differential amplifier also tends to reject the part of the input signals that are common to both inputs $(V_{in+} + V_{in-})/2$. This is referred to as the common mode signal.


[illegible]

Schematic Entry

Parameters

Library name	Cell Name	Properties/Comments
gpd180	Nmos	Model Name = nmos1 (NM0, NM1) ; W= 3u ; L =1u
gpd180	Nmos	Model Name =nmos1 (NM2, NM3) ; W=4.5u;L=1u
gpd180	Pmos	Model Name =pmos1 (PM0, PM1); W= 15u ; L= 1u

Symbol Creation

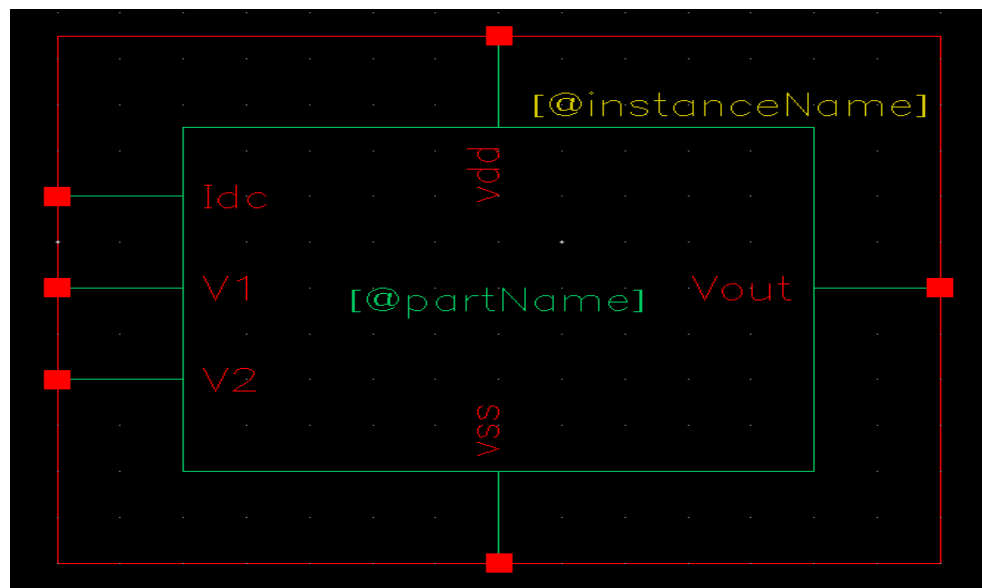


Building the Diff_amplifier_testCircuit

Using the component list and Properties/Comments in this table, build the Diff_amplifier_test schematic

Library name	Cellview name	Properties/Comments
myDesignLib	Diff_amplifier	Symbol
analogLib	vsin	Define specification as AC Magnitude= 1; Amplitude= 5m; Frequency= 1K


analogLib	vdd, vss, gnd	Vdd=2.5 ; Vss= -2.5
analogLib	Idc	Dc current = 30u

Schematic Diagram of the test circuit:

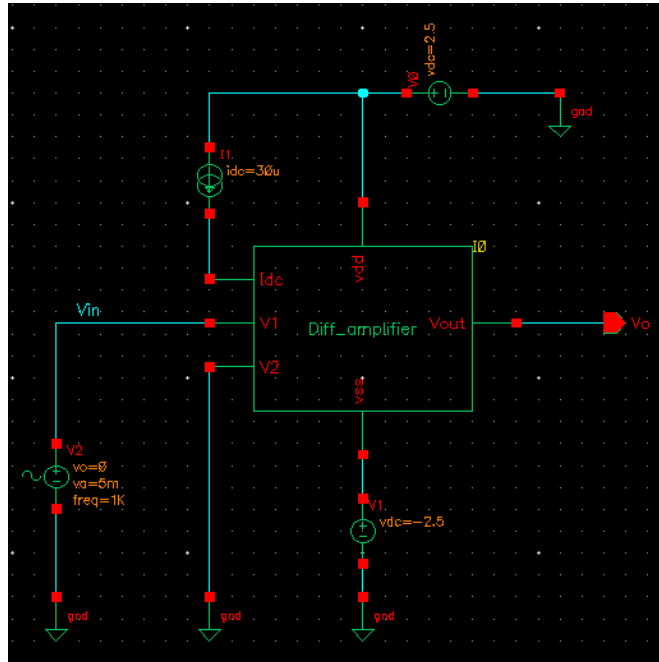


Running the Simulation

 1. Execute **Simulation – Netlist and Run** in the simulation window to start the simulation, this will create the netlist as well as run the simulation. When simulation finishes, the Transient, DC and AC plots automatically will be popped up along with netlist.



Layout

 

RESULT:

- The schematic for the differential Amplifier is drawn and verified the following: DC Analysis, DC Analysis, and Transient Analysis.
- The Layout for the differential amplifier is drawn and verified the DRC, LVS, and RC Extraction.

Lab 3: OPERATIONAL AMPLIFIER

AIM:

To simulate the schematic of the Operational Amplifier, and then to perform the physical verification for the layout of the same

TOOL REQUIRED: Cadence Tool

THEORY:


An operational amplifier (often op-amp or opamp) is a DC-coupled high-gain electronic voltage amplifier with a differential input and, usually, a single-ended output. In this configuration, an op-amp produces an output potential (relative to circuit ground) that is typically hundreds of thousands of times larger than the potential difference between its input terminals.

The popularity of the op-amp as a building block in analog circuits is due to its versatility. Due to negative feedback, the characteristics of an op-amp circuit, its gain, input and output impedance, bandwidth etc. are determined by external components and have little dependence on temperature coefficients or manufacturing variations in the op-amp itself.

Op-amps are among the most widely used electronic devices today, being used in a vast array of consumer, industrial, and scientific devices. Op-amps may be packaged as components, or used as elements of more complex integrated circuits.

The op-amp is one type of differential amplifier. The amplifier's differential inputs consist of a non-inverting input (+) with voltage V_+ and an inverting input ($-$) with voltage V_- ; ideally the op-amp amplifies only the difference in voltage between the two, which is called the differential input voltage. The output voltage of the opamp V_{out} is given by the equation: $V_{out} = AOL (V_+ - V_-)$ where AOL is the open-loop gain of the amplifier (the term "open-loop" refers to the absence of a feedback loop from the output to the input).

Schematic Capture

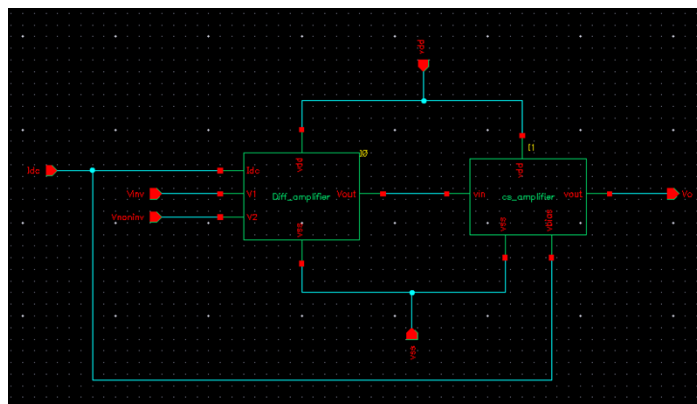

Schematic Entry


This is a table of components for building the Operational Amplifier schematic.

Library name	Cell Name	Properties/Comments
myDesignLib	Diff_amplifier	Symbol
myDesignLib	cs_amplifier	Symbol

Type the following in the ADD pin form in the exact order leaving space between the pin names.

Pin Names	Direction
Idc, Vinv, Vnoninv	Input
Vo	Output
vdd, vss	Input

Symbol Creation

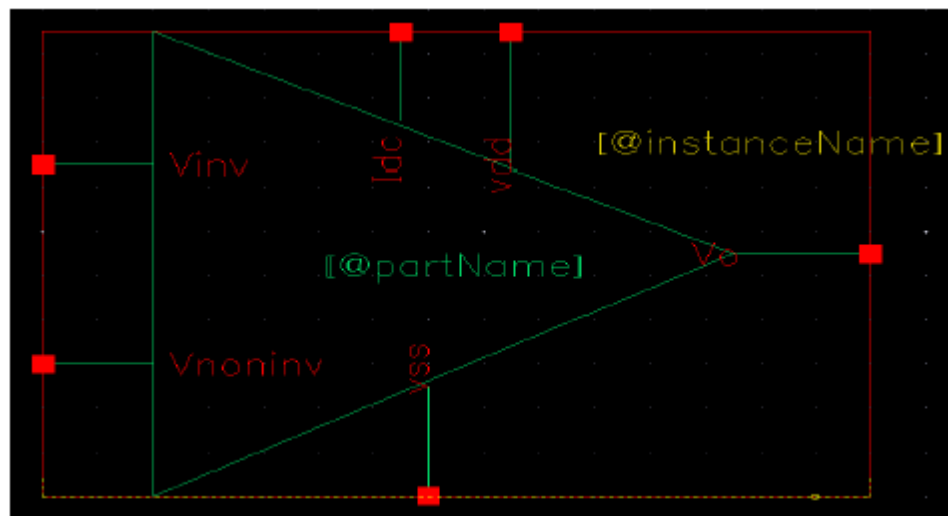


Library name	Cellview name	Properties/Comments
myDesignLib	op-amp	Symbol
analogLib	vsin	Define pulse specification as AC Magnitude= 1; DC Voltage= 0; Offset Voltage= 0; Amplitude= 5m; Frequency= 1K
analogLib	vdc, gnd	vdd=2.5 ; vss= -2.5
analogLib	Idc	Dc current = 30u


Building the Operational Amplifier Test Design

Using the component list and Properties/Comments in the table, build the op-amp_test schematic as shown below.

Library name	Cellview name	Properties/Comments
myDesignLib	op-amp	Symbol
analogLib	vsin	Define pulse specification as AC Magnitude= 1; DC Voltage= 0; Offset Voltage= 0; Amplitude= 5m; Frequency= 1K
analogLib	vdc, gnd	vdd=2.5 ; vss= -2.5
analogLib	ldc	Dc current = 30u

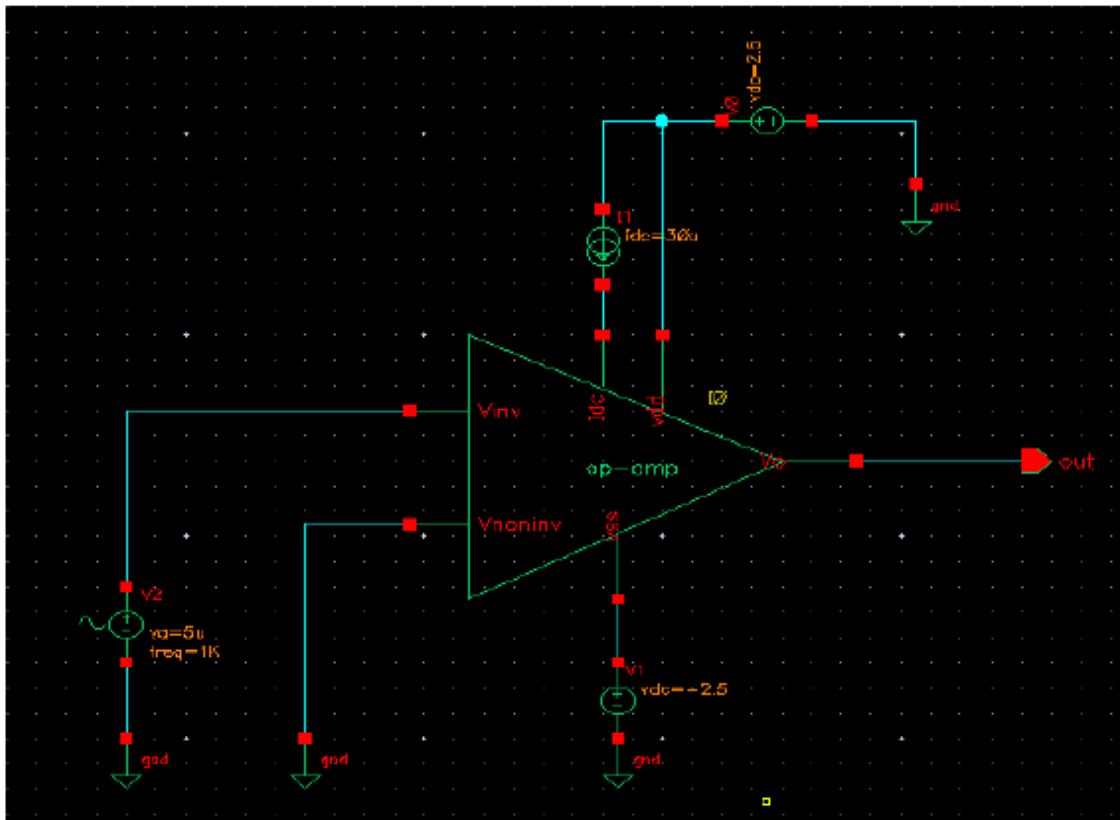


Analog Simulation with Spectre

 

Creating a layout view of Operational Amplifier

Complete the DRC, LVS check using the assura tool.

 Extract RC parasites for back annotation and Re-simulation.



RESULT:

- The schematic for the Operational Amplifier is drawn and verified the following: DC Analysis, DC Analysis, and Transient Analysis.
- The Layout for the operational amplifier is drawn and verified the DRC, LVS, and RC Extraction.

Lab 3: R-2R DAC

AIM:

To simulate the schematic of the R-2R DAC, and then to perform the physical verification for the layout of the same.


TOOL REQUIRED: Cadence Tool

THEORY:

The R-2R resistor ladder network directly converts a parallel digital symbol/word into an analog voltage. Each digital input (b0, b1, etc.) adds its own weighted contribution to the analog output. This network has some unique and interesting properties.

- Easily scalable to any desired number of bits
- Uses only two values of resistors which make for easy and accurate fabrication and integration
- Output impedance is equal to R, regardless of the number of bits, simplifying filtering and further analog signal processing circuit design

Schematic Capture

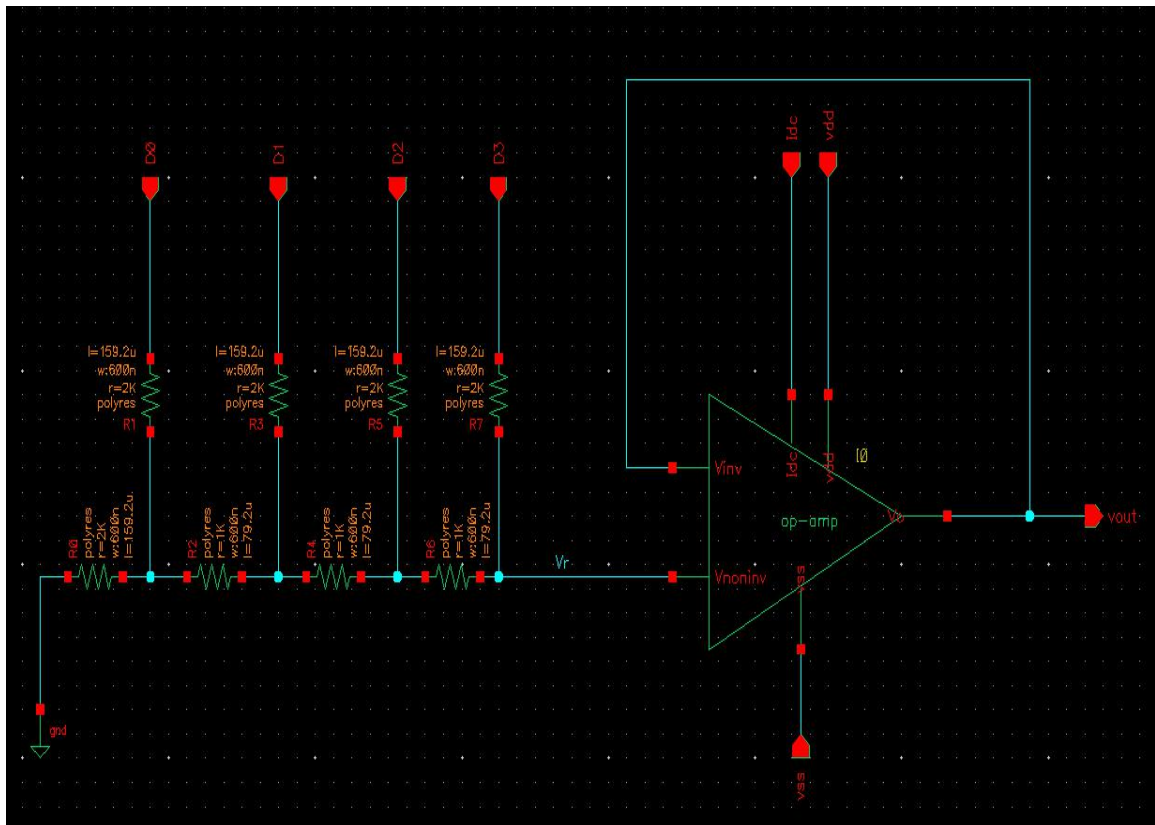

Schematic Entry

Use the techniques learned in the Lab1 and Lab2 to complete the schematic of R-2R DAC.

This is a table of components for building the R-2R DAC schematic.

Library name	Cell Name	Properties/Comments
gpd180	polyres	R = 2k
gpd180	polyres	R = 1k
MyDesignLib	op-amp	Symbol
analogLib	Idc, gnd	idc = 30u

Type the following in the ADD pin form in the exact order leaving space between the pin names.

Pin Names	Direction
Do D1 D2 D3	Input
Vout	Output
vdd, vss	Input

Symbol Creation

Use the techniques learned in the Lab1 and Lab2 to complete the symbol of R-2R DAC.




Building the R-2R DAC Test Design

Using the component list and Properties/Comments in the table, build the R-2R-DAC_test schematic as shown below.



Library name	Cellview name	Properties/Comments
myDesignLib	R-2R-DAC	Symbol
analogLib	vpulse	For V0: v1= 0 v2= 2 Ton = 5n T = 10n For V1: v1= 0 v2= 2 Ton = 10n T = 20n For V2: v1= 0 v2= 2 Ton = 20n T = 40n For V3: v1= 0 v2= 2 Ton = 40n T = 80n
analogLib	vdc, gnd	vdd = 2 vss = -2

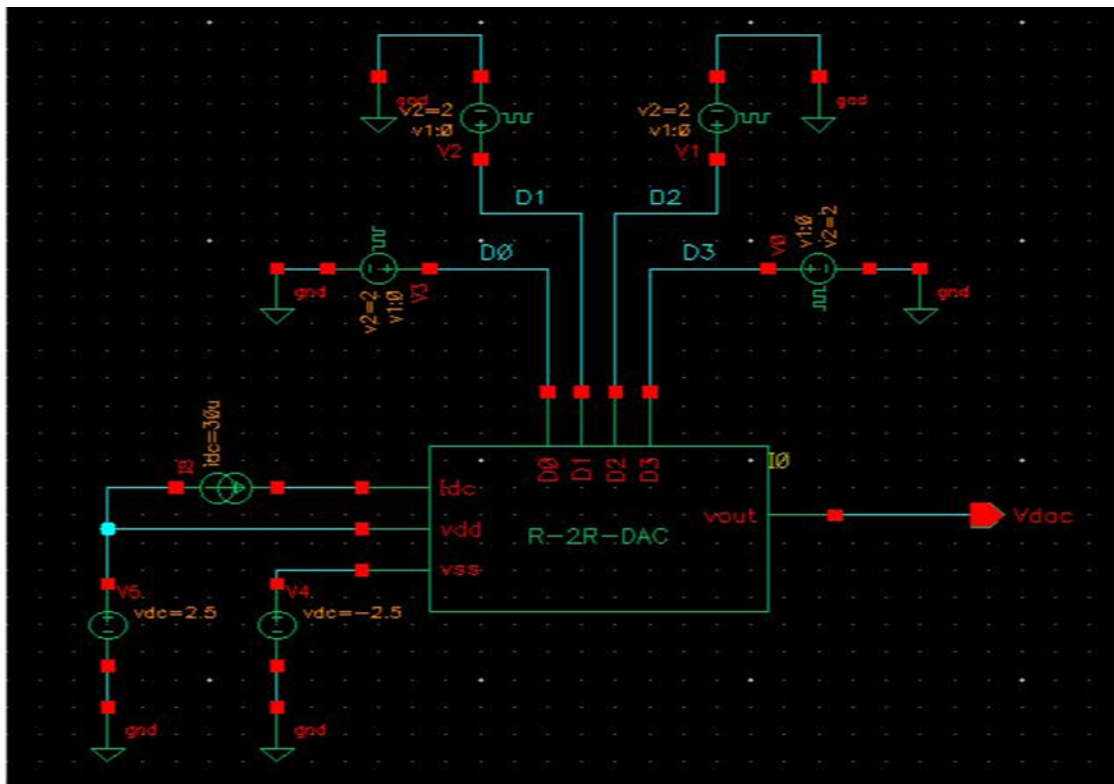Note: Remember to set the values for **vdd** and **vss**. Otherwise your circuit will have nopower.



Analog Simulation with Spectre

 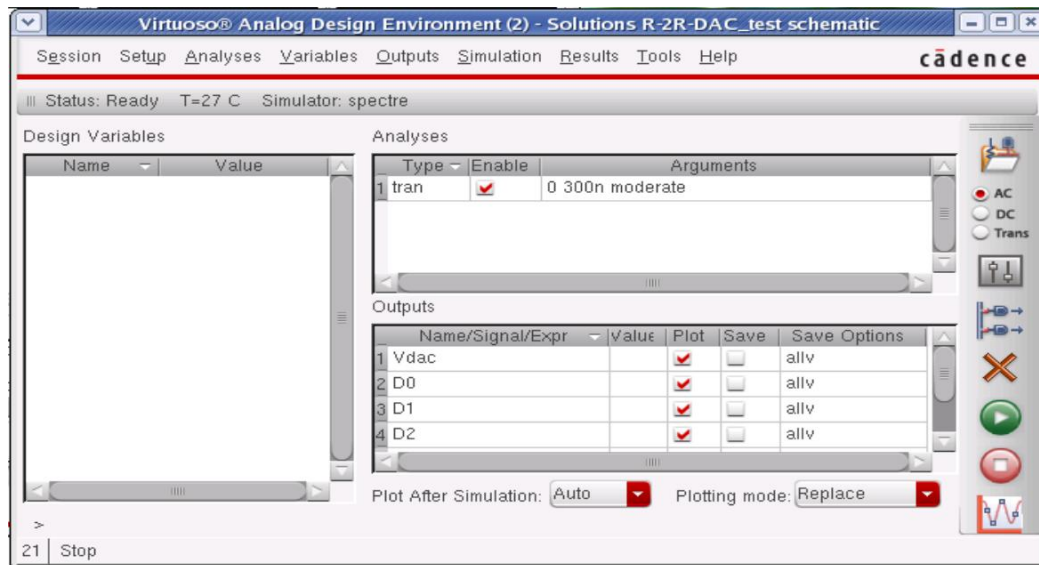Use the techniques learned in the Lab1 and Lab2 to complete the simulation of R-2R-DAC and ADE window and waveform should look like below.




Creating a layout view of R-2R DAC

Use the techniques learned in the Lab1 and Lab2 to complete the layout of R-2R-DAC.

Complete the DRC, LVS check using the assura tool.

 Extract RC parasites for back annotation and Re-simulation.



RESULT:

- 1.The schematic for the operational amplifier is drawn and verified the following:
DC Analysis, DC Analysis, Transient Analysis.
- 2.The Layout for the operational amplifier is drawn and verified the DRC, LVS, RC Extraction.

VIVA QUESTIONS

1. Why don't we use just one NMOS or PMOS transistor as a transmission gate?
2. What are set up time & hold time constraints? What do they signify?
3. Explain Clock Skew?
4. Why is NAND gate preferred over NOR gate for fabrication?
5. What is Body Effect?
6. Why is the substrate in NMOS connected to Ground and in PMOS to VDD?
7. What is the fundamental difference between a MOSFET and BJT ?
8. Why PMOS and NMOS are sized equally in a Transmission Gates?
9. What happens when the PMOS and NMOS are interchanged with one another in an inverter?
10. Why are pMOS transistor networks generally used to produce high signals, while nMOS networks are used to product low signals?
11. What is Latch Up? Explain Latch Up with cross section of a CMOS Inverter. How do you avoid Latch Up?
12. Difference between Synchronous and Asynchronous reset.
13. What is DRC ?
14. What is LVS ?
15. What is RCX ?
16. What are the differences between SIMULATION and SYNTHESIS?
17. What is a counter?
18. What are the differences between flip-flop and latch?
19. How can you convert JK flip-flop into Jk?
20. What are different types of adders?
21. Give the excitation table for JK flip-flop?
22. Give the excitation table for SR flip-flop?
23. Give the excitation table for D flip-flop?
24. Give the excitation table for T flip-flop?
25. What is the race around condition?
26. What is an amplifier?
27. What is an op-amp?
28. What is differential amplifier?
29. What is elaboration?
30. What is transient analysis?
31. What is DC analysis?
32. What is AC analysis?